

Solution to Final Exam June 2010  
Measurements 1st Elect.

$$(1) (b) R_t = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{250} + \frac{1}{500} + \frac{1}{375}}$$
$$= 115.4 \Omega$$

$$\Delta R_1 = 0.025 \times 25 = 6.25 \Omega$$

$$R_1 = 250 + 6.25 = 256.25 \Omega$$

Similarly:

$$\Delta R_2 = -0.036 \times 500 = -18 \Omega$$

$$R_2 = 500 - 18 = 482 \Omega$$

$$\Delta R_3 = 0.014 \times 375 = 5.25 \Omega$$

$$R_3 = 375 + 5.25 = 380.25 \Omega$$

Therefore:


$$R_t = \frac{1}{\frac{1}{256.25} + \frac{1}{482} + \frac{1}{380.25}} = 116.3 \Omega$$

$$\frac{\Delta R_t}{R_t} = \frac{116.3 - 115.4}{115.4} = 0.00776$$

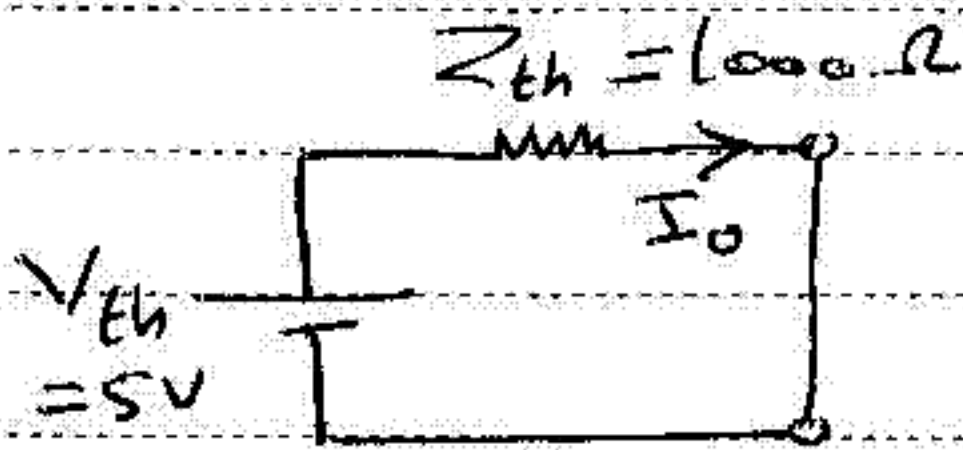(2) (a) Reduce the actual circuit to an equivalent  
Thevenin's.


$$V_{th} = V_{oc} = 10 - \frac{10}{1000 + 1000} \times 1000 = 5 \text{ V}$$

$$Z_{th} = \frac{1000 \times 1000}{1000 + 1000} + 500 = 1000 \Omega$$



$$\begin{aligned} \text{Actual current } I_0 &= \frac{V_{th}}{Z_{th}} \\ &= \frac{5}{1000} \text{ A} = 5 \text{ mA} \end{aligned}$$

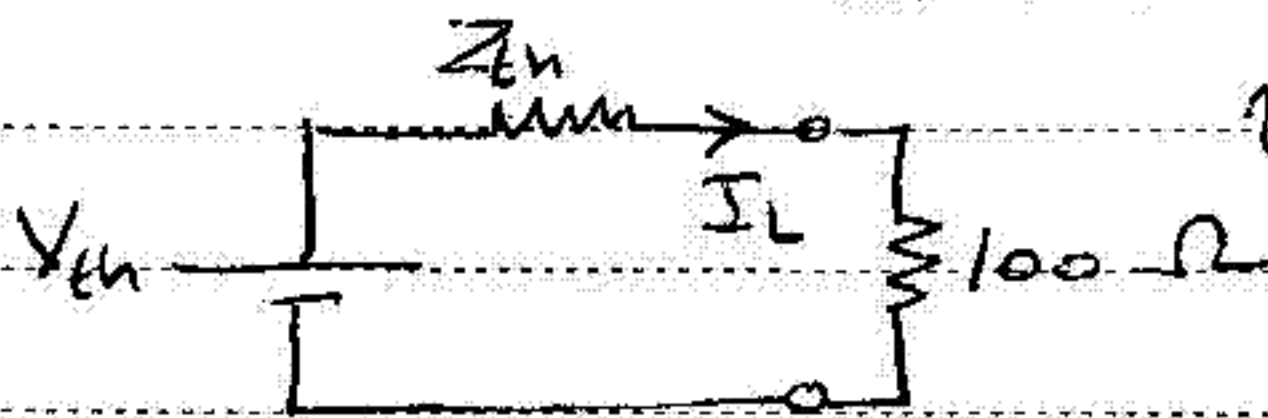When the ammeter is introduced, then measured



value is:

$$I_L = \frac{V_{th}}{Z_{th} + Z_L} = \frac{5}{1000 + 100} = 4.55 \text{ mA}$$

$$\begin{aligned} \text{Error} &= \frac{4.55 - 5}{5} \times 100 = -9\% \\ &= 9\% \text{ low} \end{aligned}$$

$$\text{Accuracy of measurement} = 100 - 9 = 91\%$$

(b) The total shunt resistance  $R_{sh}$  is:

$$R_{sh} = \frac{R_m}{n-1} = \frac{1 \times 10^3}{100-1} = \frac{1000}{99} = 10.1 \Omega$$

This is  $R_{sh}$  for the 10-mA range.

When the meter is set on the 100-mA range

$$R_b + R_c = \frac{I_m (R_{sh} + R_m)}{I_2}$$

$$= \frac{100 \times 10^{-6} \times (10.1 + 1 \times 10^3)}{100 \times 10^{-3}} = 1.01 \Omega$$

The resistance  $R_c$ , which provides the shunt resistance on the 1-A range is:

$$R_c = \frac{I_m (R_{sh} + R_m)}{I_3}$$

$$= \frac{100 \times 10^{-6} \times (10.1 + 1 \times 10^3)}{1} = 0.101 \Omega$$

$$\therefore R_b = (R_b + R_c) - R_c = 1.01 - 0.101 = 0.909 \Omega$$

$$R_a = R_{sh} - (R_b + R_c)$$

$$= 10.1 - (0.909 + 0.101) = 9.09 \Omega$$

check:

$$R_{sh} = R_a + R_b + R_c$$

$$= 9.09 + 0.909 + 0.101 = 10.1 \Omega$$

(3) (b) To Calculate  $V_{th}$ :

$$V_{th} = E \left( \frac{R_3}{R_3 + R_1} - \frac{R_4}{R_4 + R_2} \right)$$

$$= 6 \times \left( \frac{3.5}{3.5 + 1} - \frac{7.5}{7.5 + 1.6} \right)$$

$$= 6 \times (0.778 - 0.824) = 0.276 \text{ V}$$

To Calculate  $R_{th}$ :

$$R_{th} = \frac{R_1 R_3}{R_1 + R_3} + \frac{R_2 R_4}{R_2 + R_4}$$

$$= \frac{1 \times 3.5}{1 + 3.5} + \frac{1.6 \times 7.5}{1.6 + 7.5} = 2.097 \text{ k}\Omega$$

$$I_g = \frac{V_{th}}{R_{th} + R_g} = \frac{0.276}{2.097 + 200} = 120 \mu\text{A}$$

Deflection of the galvanometer  $\theta$

$$\theta = S' \times I_g = 1 \times 120 = 120 \text{ mm}$$

Sensitivity of bridge =  $\frac{\theta}{\Delta R}$

$$R_4 \text{ for balanced condition} = \frac{1.6 \times 3.5}{1} = 5.6$$

$$\Delta R = 7.5 - 5.6 = 1.9 \text{ k}\Omega$$

$$\therefore \text{Sensitivity} = \frac{120}{1.9} = 63.16 \text{ mm/k}\Omega$$

(4) (b) Reduce the circuit to its Thevenin's equivalent

$$V_{th} = 100 \times \frac{200}{400} = 50 \text{ V}$$

$$R_{th} = \frac{200 \times 200}{200 + 200} = 100 \text{ k}\Omega$$

Voltage appearing under loading conditions  $E$  is

$$E = \frac{50}{(100 + 1000) \times 10^3} = 45.45 \text{ V}$$

$$\text{Loading error} = \frac{45.45 - 50}{50} \times 100 = -9.1\%$$

= 9.1% low

$$\text{Accuracy} = 100 - 9.1 = 90.9\%$$

(c) The equivalent resistance of the volt meter on its 50 V scale is

$$R_v = 100 \times 50 = 5 \text{ k}\Omega$$

Let  $R_p$  = the parallel resistance of  $R_x$  and  $R_v$

$$R_p = \frac{V_p}{V_s} \times R_s = \frac{4.65}{95.35} \times 100 = 4.878 \text{ k}\Omega$$

Then

$$R_x = \frac{R_p \times R_v}{R_v - R_p} = \frac{4.878 \times 5}{0.122} = 200 \text{ k}\Omega$$