

Solution to Final Exam June 2010

Elect. Power Eng. 2nd year Com.

$$(1)(b) \quad A = D = 1 + \frac{YZ}{2}$$

$$= 1 + \frac{1}{2} (35 + j140) (930 \times 10^{-6})$$

$$= 0.935 + j0.0163 = 0.935 \angle 1^\circ$$

$$B = Z = 35 + j140 = 144.5 \angle 75.8^\circ \Omega$$

$$C = Y \left(1 + \frac{ZY}{4} \right) = 900 \times 10^{-6} \angle 90.5^\circ \text{ S}$$

$$= -7.57 \times 10^{-6} + j900 \times 10^{-6} \text{ S}$$

$$V_R = \frac{220}{\sqrt{3}} = 127 \text{ kV}$$

$$P_R = \sqrt{3} V_L I_L \cos \theta$$

$$40 \times 10^6 = \sqrt{3} \times 220 \times 10^3 \times I_L \times 0.9$$

$$\therefore I_L = 116.5 \angle -25.8^\circ \text{ A} = 105 - j50.6 \text{ A}$$

$$V_S = AV_R + BI_R$$

$$= 0.935 \angle 1^\circ \times 127 \times 10^3 + 144.5 \angle 75.8^\circ \times 116.5 \angle -25.8^\circ$$

$$= 129.75 + j15 = 131 \angle 6.6^\circ \text{ kV (phase-to-neutral)}$$

$$= 227 \angle 6.6^\circ \text{ kV (line-to-line)}$$

$$I_S = CV_R + DI_R$$


$$= 900 \times 10^{-6} \angle 90.5^\circ \times 127 \times 10^3 + 0.935 \angle 1^\circ \times 116.5 \angle -25.8^\circ$$

$$= 98.065 + j68.31 = 119.8 \angle 35^\circ$$


$$P_S = \sqrt{3} V_S I_S \cos \theta = \sqrt{3} \times 227 \times 119.8 \times 0.88 = 41.2 \text{ MW}$$

$$\eta = \frac{P_R}{P_S} \times 100 = \frac{40}{41.2} \times 100 = 97.3\%$$
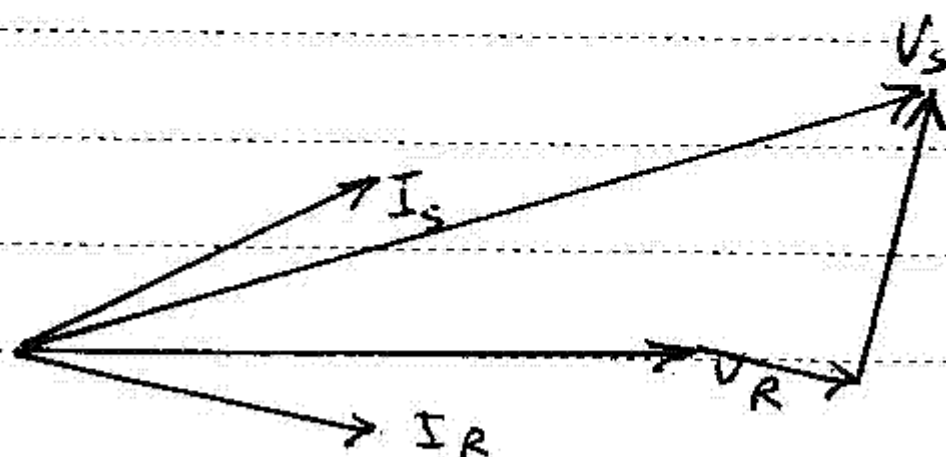
$$\% \epsilon = \frac{V_S - V_R}{V_R} \times 100 = \frac{227 - 220}{220} \times 100 = 2.75\%$$



(c)

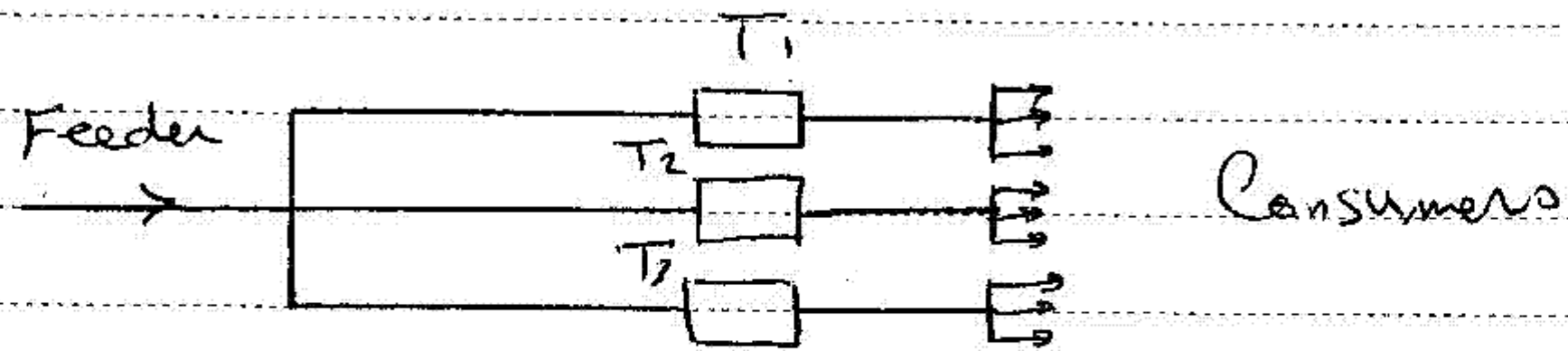

$$\begin{aligned}\text{Max Demand on } T_1 &= \text{Connected load} \times \text{demand factor} \\ &= 10 \times 0.65 = 6.5 \text{ kW}\end{aligned}$$

$$\text{Max Demand on } T_1 = \frac{6.5}{1.5} = 4.33 \text{ kW}$$

$$\text{Max Demand on } T_2 = \frac{12 \times 0.6}{3.5} = 2.057 \text{ kW}$$

$$\text{Max Demand on } T_3 = \frac{15 \times 0.7}{1.5} = 7 \text{ kW}$$

$$\text{Max Demand on Feeder} = \frac{4.33 + 2.057 + 7}{1.3}$$

$$= 10.3 \text{ kW}$$

(2)(c) Total Lumen Required = $35 \times 100 \times 20 = 70000$ Lumen

Lamp Lumen Required = $\frac{70000}{0.55 \times 0.85} = 149732.6$ Lumen

Assuming 200 W lamp, the number of lamps required is

$$N = \frac{149732.6}{200 \times 15} = 49.9 \text{ Lamp}$$

The lamps will be assumed as:

4 rows of 12 lamps each

Thus max spacing = $\frac{100}{12}$ m

$$\frac{s}{h} = \frac{100}{12 \times 4} = 2.08 > 1.5$$

Let number of lamps = $4 \times 13 = 52$ lamp

$$\frac{s}{h} = \frac{100}{13 \times 4} = 1.9 > 1.5$$

Let number of lamps = $4 \times 15 = 60$ lamp

$$\frac{s}{h} = \frac{100}{15 \times 4} = 1.6$$

Let number of lamps = $4 \times 16 = 64$ lamp

$$\frac{s}{h} = \frac{100}{16 \times 4} = 1.56 \checkmark$$

$$(3)(b) \quad d = 2.5 \text{ cm} \quad \text{and} \quad D = 6 \text{ cm}$$

$$\frac{D}{d} = \frac{6}{2.5} = 2.4 = \alpha^3$$

$$\therefore \alpha = \sqrt[3]{2.4} = 1.34$$

$$\therefore \alpha = \frac{d_1}{d} = \frac{d_2}{d_1} = \frac{D}{d_2}$$

$$\therefore 1.34 = \frac{d_1}{2.5}$$

$$d_1 = 2.5 \times 1.34 = 3.35 \text{ cm}$$

$$d_2 = 3.35 \times 1.34 = 4.489 \text{ cm}$$

$$V_{\text{peak}} = \frac{66}{\sqrt{3}} \times \sqrt{2} = 53.8 \text{ kV}$$

$$V_2 = \frac{V}{1 + \frac{1}{\alpha} + \frac{1}{\alpha^2}} = \frac{53.8}{1 + \frac{1}{1.34} + \frac{1}{(1.34)^2}} = \frac{53.8}{2.305} = 23.34 \text{ kV}$$

$$V_1 = V_2 \left(1 + \frac{1}{\alpha}\right) = 1.7463 \times 23.34 = 40.77 \text{ kV}$$

Without the intersheaths, the maximum stress would be

$$\frac{2V}{d \ln \frac{D}{d}} = \frac{2 \times 53.8}{2.5 \ln \frac{6}{2.5}} = 49.17 \text{ kV per cm}$$

$$\text{while the minimum stress} = 49.17 \times \frac{2.5}{6} \\ = 20.49 \text{ kV per cm}$$

When the intersheaths are used, the max. stress is

$$g_{\text{max}} = \frac{53.8}{\frac{1}{3}(1 + 1.34 + 1.79)} = 39.06 \text{ kV/cm}$$

$$(c) C_A = 3 C_S$$

$$C_S = \frac{1}{3} C_A = \frac{12.6}{3} = 4.2 \text{ } \mu\text{F}$$

$$C_B = 2 C_C + C_S$$

$$\therefore C_C = \frac{C_B - C_S}{2} = \frac{7.4 - 4.2}{2} = 1.6 \text{ } \mu\text{F}$$

$$C_N = 3 C_C + C_S = 3 \times 1.6 + 4.2 = 9 \text{ } \mu\text{F}$$

$$I_{ch} = \omega C_N V_{ph}$$

$$= 2\pi f C_N V_{ph}$$

$$= 2\pi \times 50 \times 9 \times 10^{-6} \times \frac{66 \times 10^3}{\sqrt{3}}$$

$$= 107.74 \text{ A}$$

(4) (a) Assume v_1 and a_1 be the volume and area of a section for 200 V system and v_2 and a_2 for that of 400 V system

$$P = V_1 I_1 = 200 I_1$$

$$P = V_2 I_2 = 400 I_2$$

Since P is the same

$$\therefore 200 I_1 = 400 I_2 \Rightarrow I_2 = 0.5 I_1$$

$$\text{Power loss } W_1 = 2 I_1^2 R_1$$

$$W_2 = 2 I_2^2 R_2 = 2 (0.5 I_1)^2 R_2 = 0.5 I_1^2 R_2$$

$$\therefore W_1 = W_2$$

$$2 I_1^2 R_1 = 0.5 I_1^2 R_2$$

$$\frac{R_2}{R_1} = \frac{2}{0.5} = 4$$

$$\frac{a_1}{a_2} = 4 \quad \text{and} \quad \frac{v_1}{v_2} = 4$$

$$\frac{v_2}{v_1} = \frac{1}{4} = 0.25$$


$$\% \text{ Saving in feeder copper} = \frac{v_1 - v_2}{v_1} \times 100$$

$$= \left(1 - \frac{v_2}{v_1}\right) \times 100$$

$$= (1 - 0.25) \times 100$$

$$= 75\%$$

4(c)

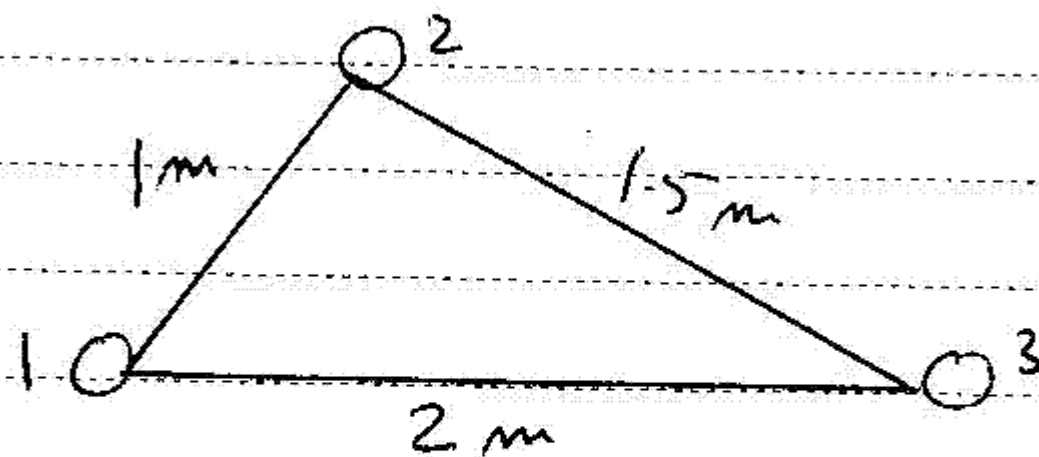

$$L = 2 \times 10^{-7} \ln \frac{GMD}{GMR}$$

$$GMD = \sqrt[3]{D_1 D_2 D_3} = \sqrt[3]{1 \times 1.5 \times 2} = 1.44 \text{ m}$$

$$GMR = 0.7788 \times 0.98 =$$

$$\therefore L = 2 \times 10^{-7} \ln \left(\frac{1.44 \times 10^2}{0.7788 \times 0.98} \right) = 10.48 \times 10^{-7} \text{ H/m}$$

$$X_L = 2\pi \times 50 \times 10.48 \times 10^{-7} = 0.329 \text{ } \Omega / \text{km / ph}$$


$$C_n = \frac{2\pi \epsilon}{\ln \frac{GMD}{GMR}} ; \quad GMD = 1.44 \text{ m} \quad GMR = r = 0.98 \text{ cm}$$

$$C_n = \frac{2\pi \times 8.85 \times 10^{-12}}{\ln \frac{1.44 \times 10^2}{0.98}} = 11.13 \times 10^{-9} \text{ F/km}$$

$$I_{ch} = 2\pi \times 50 \times 11.13 \times 10^{-9} \times \frac{132 \times 10^3}{\sqrt{3}}$$

$$= 0.267 \text{ A/km}$$

(5) (b)

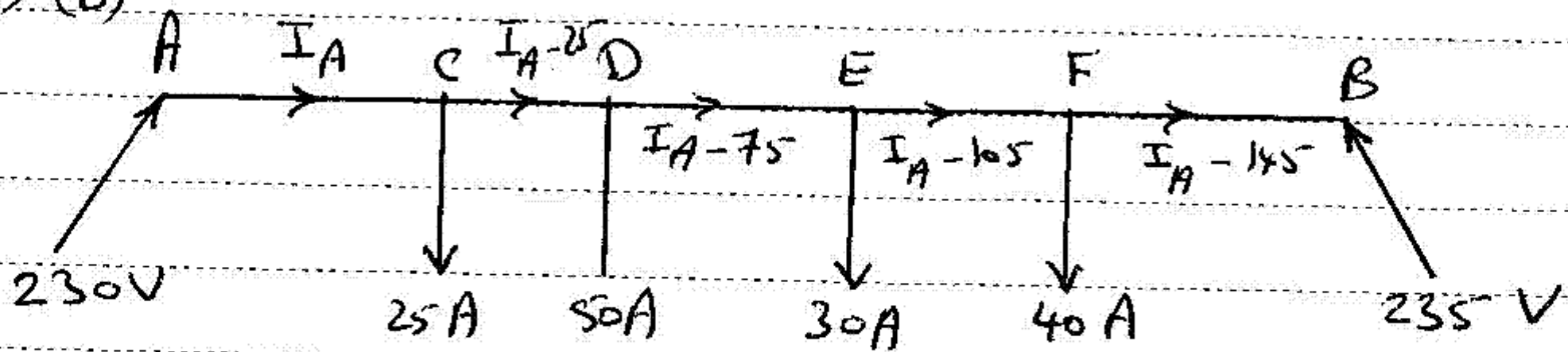

Resistance of 1000 m length of distributor (both wires)
 $= 2 \times 0.3 = 0.6 \Omega$

Resistance of section AC, $R_{AC} = 0.6 \times \frac{50}{1000} = 0.03 \Omega$

" " " CD, $R_{CD} = 0.6 \times \frac{25}{1000} = 0.015 \Omega$

" " " DE, $R_{DE} = 0.6 \times \frac{25}{1000} = 0.015 \Omega$

" " " EF, $R_{EF} = 0.6 \times \frac{50}{1000} = 0.03 \Omega$

" " " FB, $R_{FB} = 0.6 \times \frac{50}{1000} = 0.03 \Omega$

$$V_B = V_A - V_{D_{AB}}$$

$$= V_A - [I_A R_{AC} + (I_A - 25) R_{CD} + (I_A - 75) R_{DE} + (I_A - 105) R_{EF} + (I_A - 145) R_{FB}]$$

$$235 = 230 - [0.03 I_A + 0.015(I_A - 25) + 0.015(I_A - 75) + 0.03(I_A - 105) + 0.03(I_A - 145)]$$

$$235 = 230 - [0.12 I_A - 9]$$

$$I_A = \frac{239 - 235}{0.12} = 33.34 \text{ A} = I_{AC}$$

$$I_{CD} = 33.34 - 25 = 8.34 \text{ A}$$

$$I_{DE} = 33.34 - 75 = -41.66 \text{ A}$$


$$I_{EF} = 33.34 - 105 = -71.66 \text{ A}$$

$$I_{FB} = 33.34 - 145 = -111.66 \text{ A}$$

The point of min. potential is Point "D".

$$V_D = V_A - [I_{AC} R_{AC} + I_{CD} R_{CD}]$$

$$= 230 - 1.125 = 228.875 \text{ V}$$

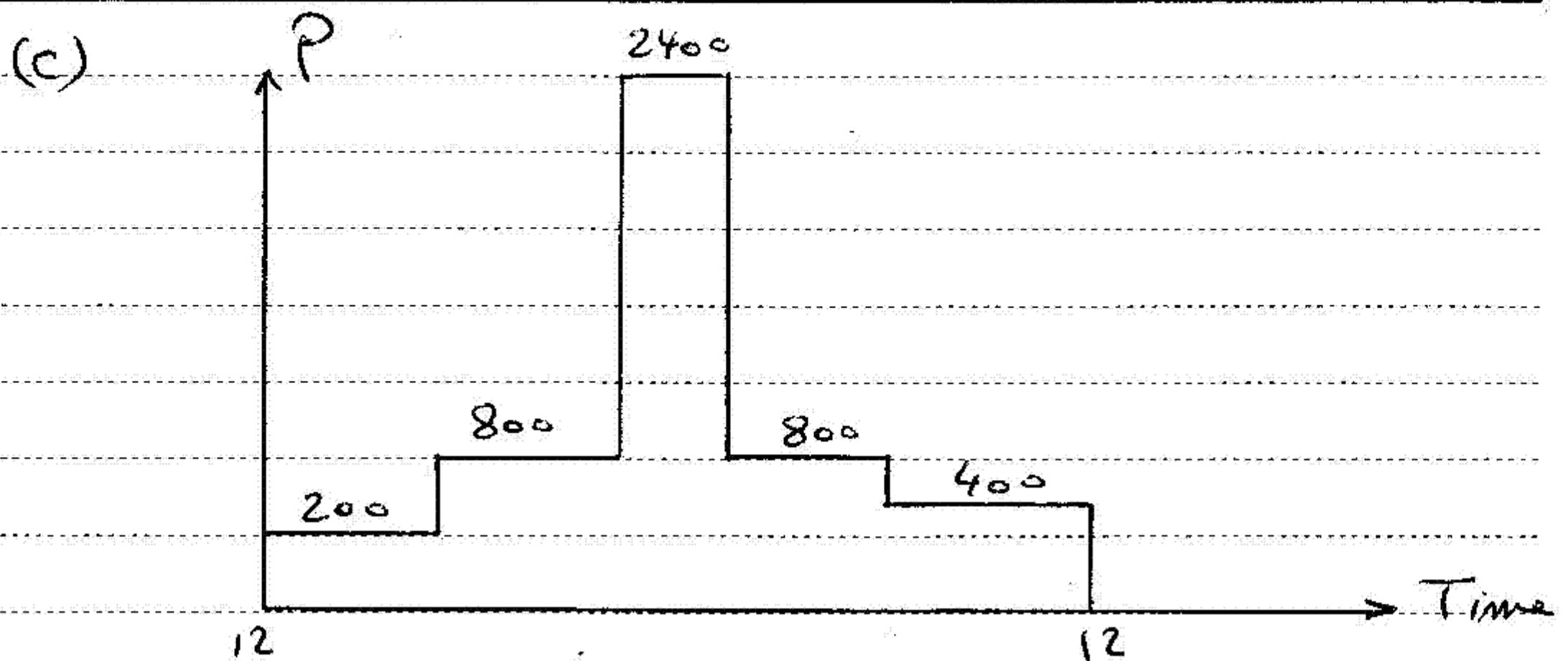

$$\text{Max Demand of Consumer 1} = 800 \text{ W}$$

$$\text{" " " " " 2} = 1000 \text{ W}$$

$$\text{" " " " " 3} = 1200 \text{ W}$$

$$\text{L.F. of Consumer 1} = \frac{600 \times 6 + 200 \times 2 + 800 \times 6}{800 \times 24} \times 100 = 45.8\%$$

$$\text{" " Consumer 2} = \frac{200 \times 8 + 1000 \times 2 + 200 \times 2}{1000 \times 24} \times 100 = 16.7\%$$

$$\text{" " Consumer 3} = \frac{200 \times 6 + 1200 \times 2 + 200 \times 2}{1200 \times 24} \times 100 = 13.8\%$$

$$\text{Siml Max Demand on the Station} = 200 + 1000 + 1200 = 2400 \text{ MW}$$

$$\text{Diversity factor} = \frac{800 + 1000 + 1200}{2400} = 1.25$$

$$\text{Station Load Factor} = \frac{\text{Total Energy Consumed / day}}{\text{Siml Max Demand} \times 24}$$

$$= \frac{8800 + 4000 + 4000}{2400 \times 24} \times 100$$

$$= 29.1\%$$