


Solution for the final exam for the
subject of electric circuits "ECE 102"

Fall 2009 / 2010

by: Dr. Ahmed A. Nashat

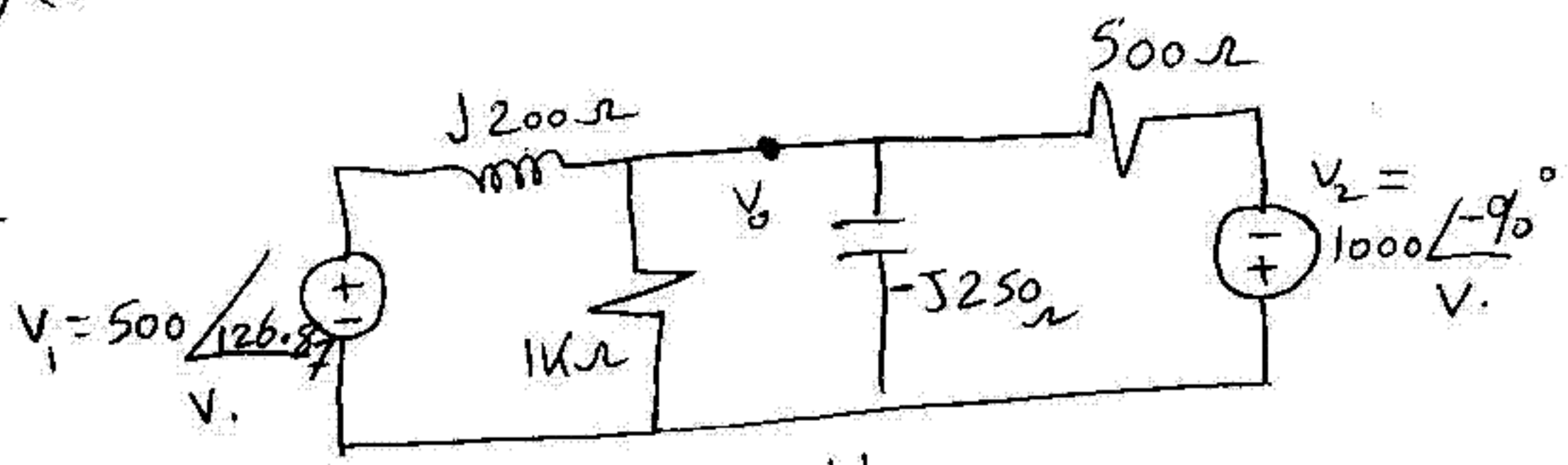Q.1. (16 points)

$L \text{ in } \Omega = j\omega L = j200 \Omega$
 $C \text{ in } \Omega = \frac{1}{j\omega C} = -j250 \Omega$



Using Nodal-Voltage method

$$\Rightarrow \frac{V_0 - V_1}{j200} + \frac{V_0}{1k} + \frac{V_0 + V_2}{500} + \frac{V_0}{-j250} = 0$$

$$\Rightarrow \frac{V_0 - 500\angle 126.87}{j200} + \frac{V_0}{1k} + \frac{V_0 + 1000\angle -90}{500} + \frac{V_0}{-j250} = 0$$

$$\Rightarrow \frac{V_0 + 3000 - j4000}{j200} + \frac{V_0}{1000} + \frac{V_0 + j1000}{500} - \frac{V_0}{j250} = 0$$

$$\Rightarrow V_0 \left\{ \frac{1}{j200} + \frac{1}{1000} + \frac{1}{500} - \frac{1}{j250} \right\} = \frac{j1000}{500} - \frac{3000}{j200} + 2$$

$$V_0 \{ 0.003 - j0.001 \} = 2 + j17$$

$$\Rightarrow V_0 = \frac{2 + j17}{0.003 - j0.001} = \frac{17.11\angle 83.3^\circ}{0.0032\angle -18.4^\circ} \approx 5346.9\angle 101.7^\circ \text{ Volt}$$

$$\Rightarrow V_0 = 5346.9 \cos(8000t + 101.7) \text{ Volt}$$


Q.2 (18 points) (10+4+4)

$$\omega = 20,000 \frac{\text{rad}}{\text{sec}}$$

$$L = j\omega L = j10 \Omega$$

$$C = \frac{1}{j\omega C} = -j40 \Omega$$

$$i_g(t) = 6 \angle 0^\circ \text{ A}$$

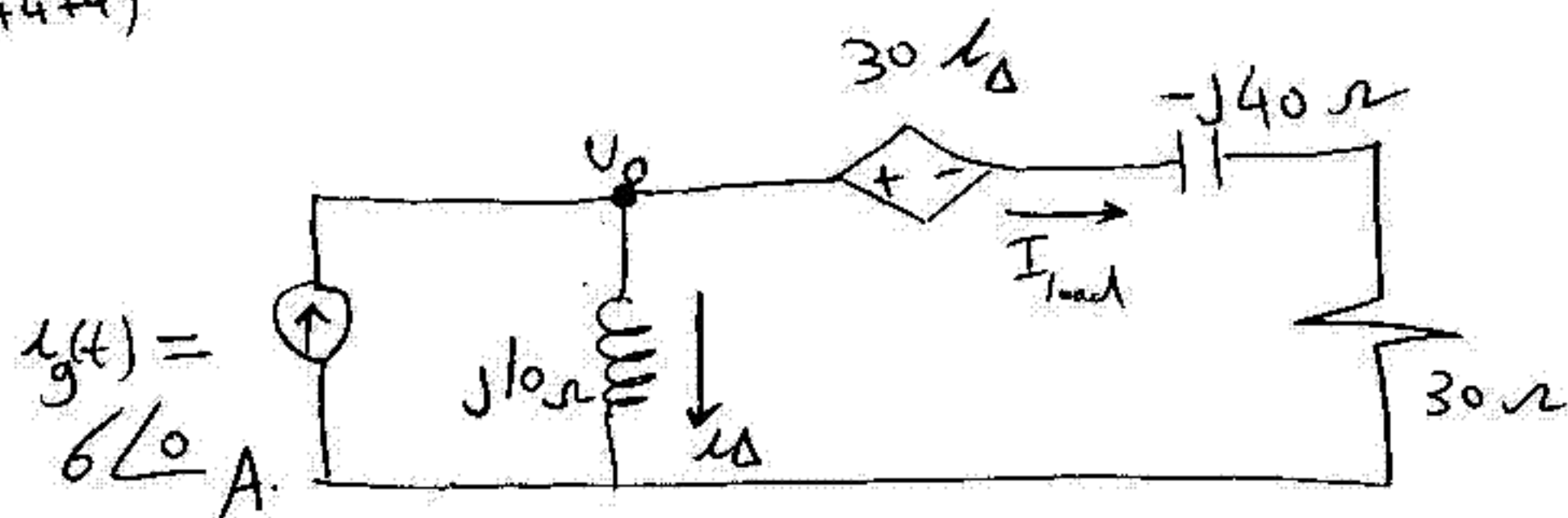

Using the nodal-voltage method

$$\Rightarrow \frac{U_0 - 30 i_\Delta}{30 - j40} + \frac{U_0}{j10} - 6 \angle 0 = 0 \quad \text{--- (1)}$$

$$\& U_0 = j10 i_\Delta \quad \text{--- (2)} \quad \text{sub. (2) in (1)}$$

$$\Rightarrow \frac{j10 i_\Delta - 30 i_\Delta}{30 - j40} + \frac{j10 i_\Delta}{j10} - 6 \angle 0 = 0$$

$$\Rightarrow i_\Delta \left\{ \frac{-30 + j10}{30 - j40} \right\} + i_\Delta = 6 \angle 0$$

$$\Rightarrow i_\Delta \left\{ \frac{-j30}{30 - j40} \right\} = 6 \angle 0$$

$$\Rightarrow i_\Delta = 8 + 6j = 10 \angle 36.87^\circ \text{ A} \quad \& U_0 = 100 \angle 126.87^\circ \text{ V}$$

(a) real & reactive power associated with $\tilde{L}'' = S_L = V_L I_L^*$
 $= 100 \angle 126.87^\circ \cdot 10 \angle -36.87^\circ = 1000 \angle 90^\circ = j1000 \text{ VA}$
 $\Rightarrow \text{real power} = 0 \quad \& \text{reactive power} = 1000 \text{ VAR}$

$\&$ real & reactive power associated with the load $(30 - j40) \Omega$ is
 $S_{\text{load}} = V_{\text{load}} I_{\text{load}}^*$ $I_{\text{load}} = 6 \angle 0^\circ - i_\Delta = 6 \angle 0^\circ - 10 \angle 36.87^\circ = \frac{6.324}{\sqrt{40}} \angle 71.565^\circ \text{ A}$

$$V_{\text{load}} = U_0 - 30 i_\Delta = 100 \angle 126.87^\circ - 300 \angle 36.87^\circ = -300 - j100 = 316.227 \angle 18.434^\circ \text{ V}$$

$$\Rightarrow S_{\text{load}} = 2000.141 \angle -53.131^\circ = 1200.056 - j1600.131 \text{ VA}$$

power associated with the source $i_g(t) = -U_0 i_g^*(t) = -100 \angle 126.87^\circ \times 6 \angle 0^\circ = -600 \angle 126.87^\circ$
 $= +360 - j480 \text{ VA}$

power associated with the $30 \angle 0^\circ$ source $= -(30 \angle 0^\circ) \cdot I_{\text{load}}^* = +897.366 \angle -34.695^\circ$
 $= -1560 + j1079.998 \text{ VA}$

- (b) real power generated = ~~reactive~~ real power absorbed
as seen from part (a) \Rightarrow the real terms add up to zero.
- (c) reactive power generated = reactive power absorbed
as seen from part (a) \Rightarrow the imaginary terms add up to zero.

Q.3. (14 points)

using nodal-voltage method

$$\frac{V_1 + 75}{6} + \frac{V_1 + 7I_{\Delta}}{12} + \frac{V_1 - V_2}{15} = 0 \quad (1)$$

$$\frac{V_2 - V_1}{15} + \frac{V_2}{60} + 1.6 I_{\Delta} = 0 \quad (2)$$


$$V_{\Delta} = V_1 + 75 \quad (3)$$

sub. (3) & (4) in (1) and (2)

$$I_{\Delta} = \frac{V_2 - V_1}{15} \quad (4)$$


get V_1 & V_2 then get V_{Δ} & I_{Δ}
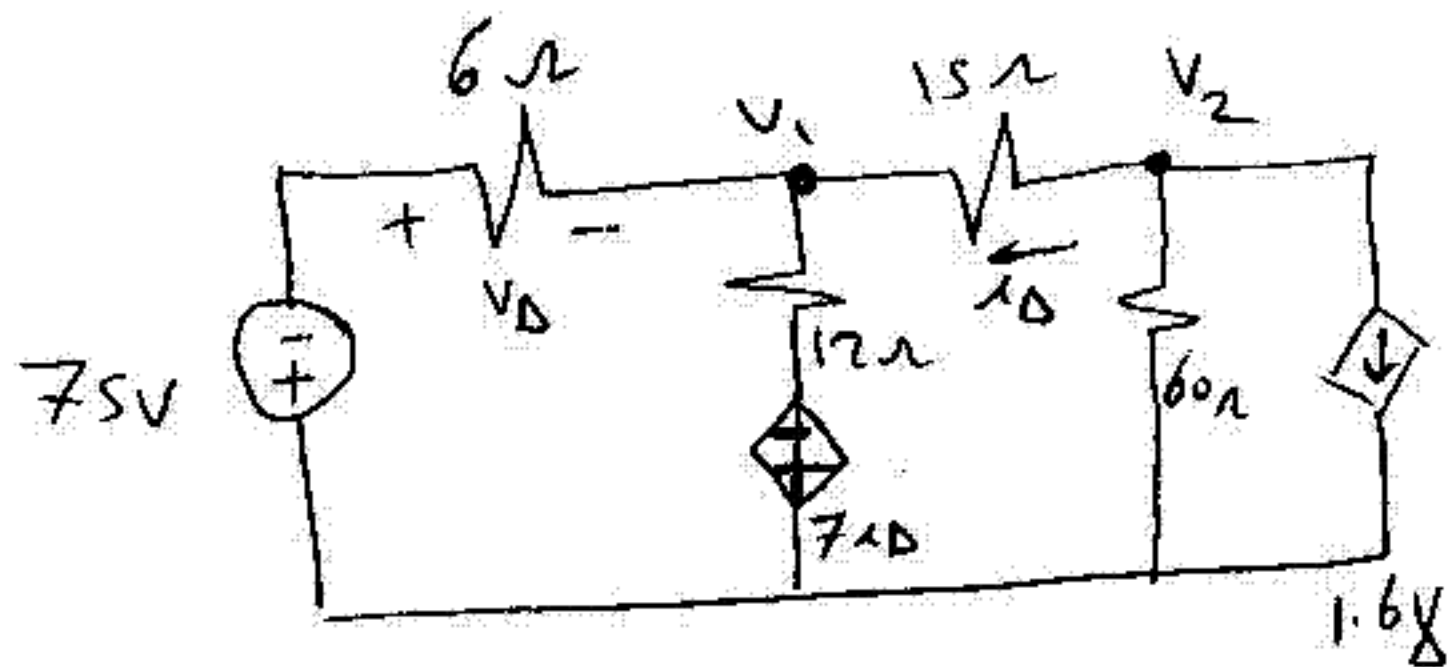
$$\Rightarrow \text{total power dissipated} = \underbrace{I_{6\Omega}^2}_{\left(\frac{V_{\Delta}}{6}\right)^2} \times 6 + \underbrace{I_{12\Omega}^2}_{\left(\frac{V_1 + 7I_{\Delta}}{12}\right)^2} \times 12 + \frac{I_{\Delta}^2}{15} \times 15 + \frac{V_2^2}{60}$$



Q.4 (18 points) (12+2+4)

(4)

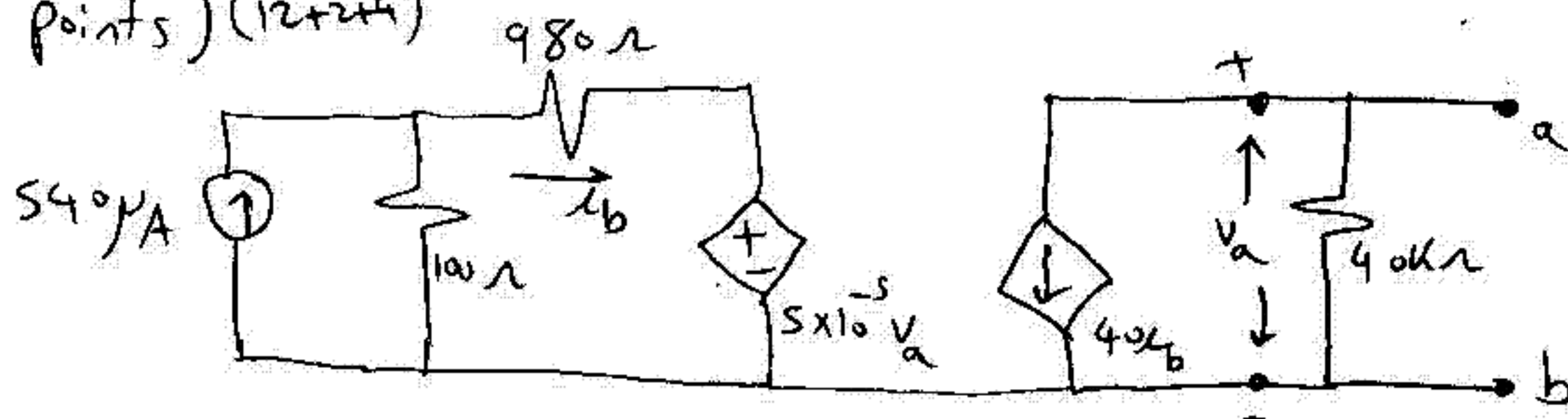

to get V_{th}

$$V_{th} = V_{ab} = -40 I_b \times 40 \text{ k}\Omega = -1600 \times 10^3 I_b \text{ V.} = V_a \quad \text{--- (1)}$$

$$I_b = \frac{54 \times 10^{-3} - 5 \times 10^{-5} V_a}{1080} \Rightarrow \text{sub in (1)}$$

$$\Rightarrow \frac{-1600 \times 10^3}{1080} \left\{ 54 \times 10^{-3} - 5 \times 10^{-5} V_a \right\} = V_a$$

$$\Rightarrow V_a = -0.864 \text{ Volt} = V_{th}$$

for R_{th}


short circuit the output and get $I_{s.c.}$

$$\Rightarrow V_a = 0 \Rightarrow I_{s.c.} = -40 I_b$$

$$I_b \text{ in this case} = \frac{540 \mu\text{A} \times 100}{100 + 980} = 50 \mu\text{A}$$

$$\Rightarrow I_{s.c.} = -40 \times 50 \mu = -2 \text{ mA}$$
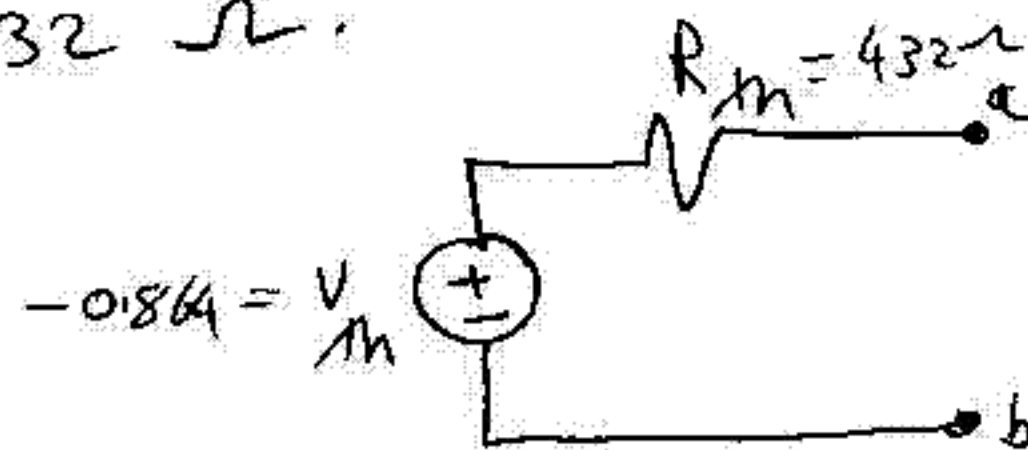
$$\Rightarrow R_{th} = \frac{V_{th}}{I_{s.c.}} = \frac{-0.864}{-2 \text{ m}} = 432 \Omega$$




(b) $R_L = R_{th} = 432 \Omega$

(c) $\text{max. power} = \frac{V_{th}^2}{4 R_L} = \frac{(-0.864)^2}{4 \times 432} = 0.432 \text{ mW}$

Q.5 (16 points) (12+4)

a) for $t \geq 0$

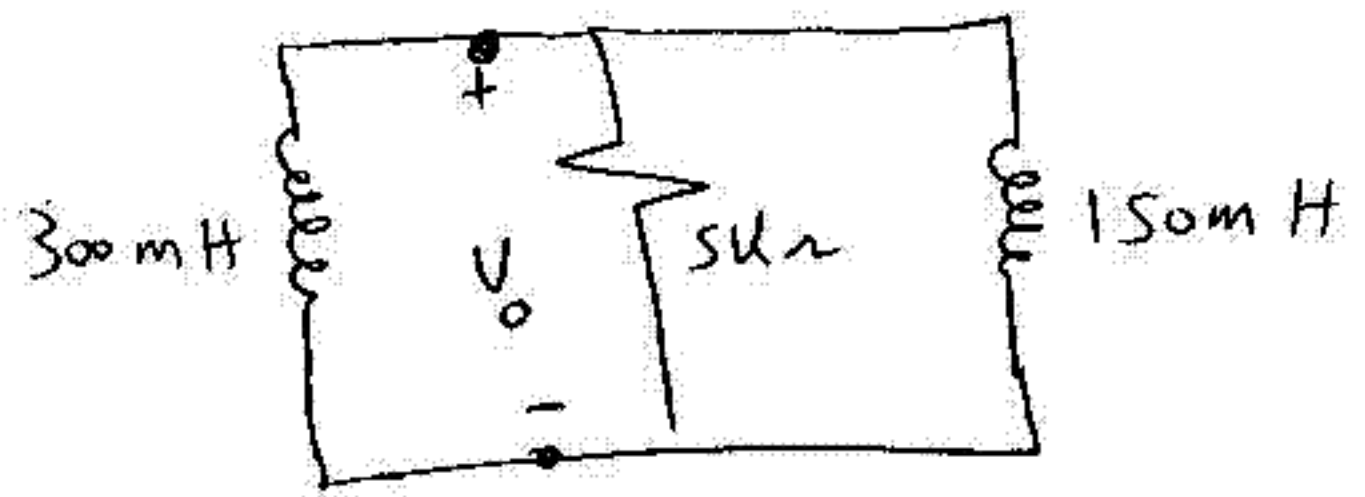

The initial current in 300mH is

$$I_0 = \frac{6 \text{ m} \times 3.2 \text{ k}\Omega}{3.2 \text{ k}\Omega + 1.6 \text{ k}\Omega} = 4 \text{ mA}$$

$$\Rightarrow v_o(t) = I_0 \cdot R e^{-t/\tau}$$

$$\tau = \frac{L}{R} = \frac{(300 \text{ m} // 150 \text{ m})}{5 \text{ k}} = \frac{\frac{300 \times 150 \text{ m}}{450}}{5 \text{ k}} = \frac{100}{5} = 25 \text{ sec}$$

$$\Rightarrow v_o(t) = (4 \times 5) e^{-0.04t} = 20 e^{-0.04t} \text{ V}$$

b) $w = \int_0^{\infty} p(t) dt = \int_0^{\infty} \frac{v_o^2(t)}{R} dt = 80 \text{ m} \int_0^{\infty} e^{-0.0016t} dt$

$$= 80 \text{ m} \left[\frac{e^{-0.0016t}}{-0.0016} \right]_0^{\infty} = \frac{80 \text{ m}}{0.0016} = 50 \text{ J}$$

Q.6 (18 points) (2+2+12+2)

a) initial value of $v_c = -\frac{40 \times 60}{60+20} = -30 \text{ V}$

final value of $v_c = 90 \text{ V}$

b) $\tau = RC = 400 \text{ }\mu\text{s} \times 0.5 \text{ }\mu\text{F} = 0.2 \text{ sec}$

c) for $t \geq 0$ $v_c(t) = 90 + (-30 - 90) e^{-5t} \text{ volt}$

$$i_c(t) = C \frac{dv_c(t)}{dt} = 0.5 \text{ }\mu\text{F} (-120) e^{-5t} \times (-5)$$

$$= 300 e^{-5t} \text{ }\mu\text{A}$$

d) $90 - 120 e^{-5t} = 0 \Rightarrow t = \frac{1}{5} \ln\left(\frac{4}{3}\right) = 57.54 \text{ m s}$