

Comm.

$$L_1 = 1414 - j1414 = 2000 \angle -45$$

$$L_2 = 1200 - j800$$

$$L_3 = 4000 + j1937$$

$$P_1 = I_1 V_1 \cos \phi \rightarrow (\theta_v - \theta_i)$$

$$1414 = I_1 100 \cos(90 - \theta_i)$$

$$S_1 = I_1^* V_1$$

$$2000 \angle -45 = I_1 100 \angle 90$$

$$I_1^* = 20 \angle -135^\circ \text{ A}$$

$$I_1 = 20 \angle 135^\circ$$

$$L_2 + L_3 = 5200 + j1139j$$

$$S = 5323.28 \angle 12.35^\circ$$

$$S = I_2^* V_2$$

$$5323.28 \angle = I_2^* 100 \angle 90$$

$$I_2^* = 53.2328 \angle -77.6^\circ$$

$$I_2 = 53.2328 \angle 77.6^\circ \text{ A}$$

$$I_0 = I_1 + \bar{I}_2 = 20 \angle 135 + 53.2 \angle 77.6$$

$$\approx 66.19 \angle 94.4^\circ \text{ A}$$

$$S_T = 6614 - j2777.3 \text{ VA}$$

$$\textcircled{2} \quad \bar{I}_1 = 31.90 \text{ A}$$


$$X_L = \omega L$$

$$M = k \sqrt{L_1 L_2}$$

$$= 0.5 \times \sqrt{\frac{10}{1000} \times \frac{10}{1000}}$$

$$= 5 \times 10^{-3} \text{ H}$$

$$\omega M = 5j$$

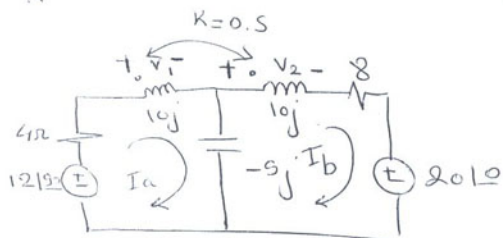

$$12\angle 90^\circ - 4 \bar{I}_a - 10j \bar{I}_a - (-5j)(\bar{I}_a - \bar{I}_b) - V_1 = 0$$

$$V_1 = + + 5j \bar{I}_b$$

$$-5j(\bar{I}_b - \bar{I}_a) + 10j \bar{I}_b + 8 \bar{I}_b + 20\angle 0^\circ + V_2 = 0$$

$$V_2 = + + 5j \bar{I}_a$$

Solve eq(1) and eq(2)

$$12j + (-4 - 10j + 5j) \bar{I}_a + (-5j + 5j) \bar{I}_b = 0$$

$$12j + (-4 - 5j) \bar{I}_a = 0 \rightarrow \bar{I}_a = \frac{-12j}{-4 - 5j}$$

$$\bar{I}_a = \frac{12\angle 90^\circ}{6.4\angle 51.3^\circ} = 1.875\angle 38.7^\circ \text{ A}$$


$$\bar{I}_2 = \bar{I}_b \quad \bar{I}_3 = \bar{I}_a - \bar{I}_b$$

$$E = \frac{1}{2} L_1 \bar{I}_a^2 + \frac{1}{2} L_2 \bar{I}_b^2 + M \bar{I}_a \bar{I}_b$$

at $t < 0$ switch opened


$$I_{L_0} = 0$$
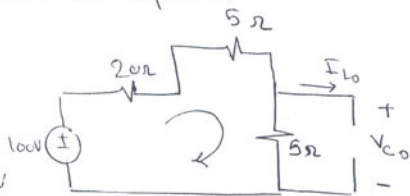
$$V_{C_0} = \frac{100 \times 5}{30} = \left(\frac{50}{3}\right) \text{ V}$$



at $t \geq 0$ switch closed
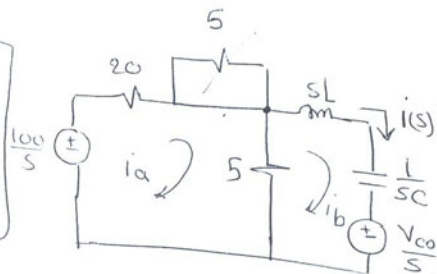
$$\left[\begin{aligned} \frac{100}{s} - 20i_a - 5(i_a - i_b) &= 0 \\ 5(i_b - i_a) + sL i_b + \frac{1}{sC} i_b + \frac{V_{C_0}}{s} &= 0 \end{aligned} \right]$$



solve 2 equations

$$\frac{100}{s} - 25i_a + 5i_b = 0 \rightarrow i_a = \frac{100}{s} + 5i_b$$

$$\frac{50}{3s} + (5 + sL + \frac{1}{sC})i_b - 5i_a = 0$$

$$s \left[\frac{50}{3s} + (5 + sL + \frac{1}{sC})i_b - \cancel{s} \left(\frac{100}{s} + 5i_b \right) \right] = 0$$

$$\frac{50}{3} + (s^2L + 5s + \frac{1}{C})i_b - (20 + 5s)i_b = 0$$

$$-\frac{10}{3} + i_b(s^2L + 4s + \frac{1}{C}) = 0$$

$$i_b = \frac{\frac{10}{3}}{s^2 L + 4s + \frac{1}{C}} = \frac{10/3}{s^2 + 4s + 25}$$

$$s = -2 \pm j\sqrt{21}$$

$$i_b = \frac{10/3}{(s+2+j\sqrt{21})(s+2-j\sqrt{21})} = \frac{k}{(\quad)} + \frac{k^*}{(\quad)}$$

$$i(t) = \frac{10}{3} 2|k| e^{-2t} \cos(\sqrt{21}t + \theta)$$

$$\theta = \tan^{-1} \frac{y}{x} \text{ of } k$$

(4)

$$f(t) = \begin{cases} 7.5 & 0 < t < 1 \\ 2.5 & 1 < t < 2 \end{cases}$$

$$a_v = \frac{1}{T} \int_0^T f(t) dt = \frac{1}{2} \left[\int_0^1 7.5 dt + \int_1^2 2.5 dt \right]$$

$$= \frac{1}{2} [7.5(1-0) + 2.5(2-1)] = 5$$

$$\begin{aligned} \omega_0 &= \frac{2\pi}{T} \\ &= \frac{2\pi}{2} = \pi \end{aligned}$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt$$

$$= \frac{2}{2} \left[\int_0^1 7.5 \cos n\omega_0 t dt + \int_1^2 2.5 \cos n\omega_0 t dt \right]$$

$$= \left[7.5 \frac{\sin n\omega_0 t}{n\omega_0} \right]_0^1 + 2.5 \frac{\sin n\omega_0 t}{n\omega_0} \Big|_1^2$$

$$= \frac{7.5}{n\pi} (\sin n\pi - 0) + \frac{2.5}{n\pi} (\sin 2n\pi - \sin n\pi)$$

$$= \frac{5}{n\pi} \sin n\pi = \underline{\underline{0}}$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt$$

$$= \frac{2}{2} \left[\int_0^1 7.5 \sin n\omega_0 t dt + \int_1^2 2.5 \sin n\omega_0 t dt \right]$$


$$= 7.5 \left(-\frac{\cos n\omega_0 t}{n\omega_0} \right) \Big|_0^1 + 2.5 \left(-\frac{\cos n\omega_0 t}{n\omega_0} \right) \Big|_1^2$$

$$= -\frac{7.5}{n\pi} (\cos n\pi - 1) - \frac{2.5}{n\pi} (\cos 2n\pi - \cos n\pi)$$

$$b_n = -\frac{5}{n\pi} \cos n\pi + \frac{5}{n\pi} = \frac{5}{n\pi} (1 - \cos n\pi)$$

$$V(t) = a_v + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$
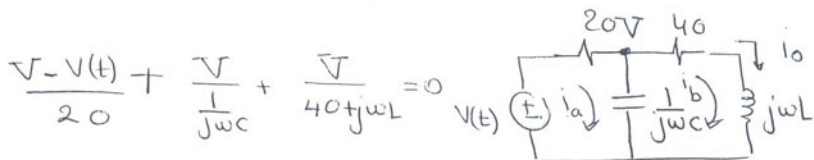
$$V(t) = 5 + \sum_{n=1}^{\infty} \frac{5}{n\pi} (1 - \cos n\pi) \sin n\omega_0 t$$



$$V \left(\frac{1}{20} + j\omega C + \frac{1}{40 + j\omega L} \right) = \frac{V(t)}{20}$$

$$V = \frac{V(t)}{1 + 20j\omega C + \frac{20}{40 + j\omega L}}$$

$$i_o = \frac{V}{40 + j\omega L} = \frac{V(t)}{(40 + j\omega L) \left[1 + 20j\omega C + \frac{20}{40 + j\omega L} \right]}$$

$$i_o = \frac{5 + \sum_{n=1}^{\infty} \frac{5}{n\pi} (1 - \cos n\pi) \sin n\omega_0 t}{(40 + j\omega L) \left[1 + 20j\omega C + \frac{20}{40 + j\omega L} \right]}$$

$$\begin{aligned}
 & \frac{5 + \sum_{n=1}^{\infty} \frac{5}{n\pi} (1 - \cos n\pi) \sin n\omega_0 t}{\underbrace{(60 + 40 \cdot j\omega - 0.1\omega^2)}_{100 \times 10^{-3}} + \underbrace{20j\omega C(40 + j\omega L)}_{50 \times 10^{-3}} + \underbrace{20}_{100 \times 10^{-3}}}
 \end{aligned}$$


$$\textcircled{5} \quad Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

to get Z_{11}

$$Z_{11} = 1 + j + \frac{1(-j)}{1-j}$$
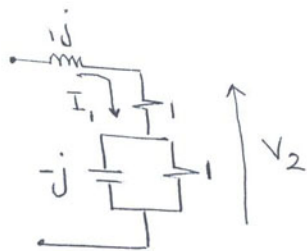
$$= \frac{-j + 1 - j^2}{1-j} = \frac{2-j}{1-j}$$



$$I_2 = 0$$

$$V_2 = \frac{V_1}{\left(\frac{2-j}{1-j}\right)} + \left(1 + \frac{-j}{1-j}\right) = V_1 \left[\frac{1-j}{2-j} - \frac{j}{2-j} \right]$$

$$= V_1 \left(\frac{1-2j}{2-j} \right)$$


$$I_1 = \frac{V_1}{Z_{11}} = \frac{V_1 (1-j)}{(2-j)}$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{V_1 (1-2j)(2-j)}{V_1 (1-j)(2-j)} = \frac{1-2j}{1-j}$$

to get Z_{22}

$$Z_{22} = -j + 1 - \frac{j}{1-j}$$
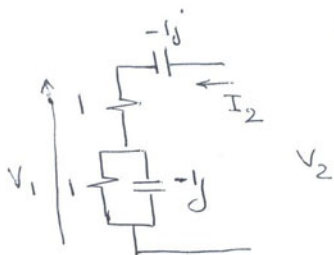
$$= \frac{-j + 1 - 2j + j^2}{1-j} = \frac{-3j}{1-j}$$



$$I_1 = 0$$

$$V_1 = \frac{V_2}{\left(\frac{-3j}{1-j}\right)} \left[1 + \frac{-j}{1-j} \right] = V_2 \left[\frac{1-j}{-3j} + \frac{-j}{-3j} \right]$$

$$= V_2 \left[\frac{1-2j}{-3j} \right]$$

$$I_2 = \frac{V_2}{Z_{22}} = \frac{V_2}{\frac{-3j}{1-j}} = \frac{V_2}{-3j} (1-j)$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{V_2 \left(\frac{1-2j}{-3j} \right)}{\frac{V_2}{-3j} (1-j)} = \frac{1-2j}{1-j}$$

$$[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \left(\frac{2-j}{1-j}\right) & \left(\frac{1-2j}{1-j}\right) \\ \left(\frac{1-2j}{1-j}\right) & \left(\frac{-3j}{1-j}\right) \end{bmatrix}$$

$$= \begin{bmatrix} 1.5 + 0.5j & 1.5 - 0.5j \\ 1.5 - 0.5j & 1.5 - 1.5j \end{bmatrix}$$