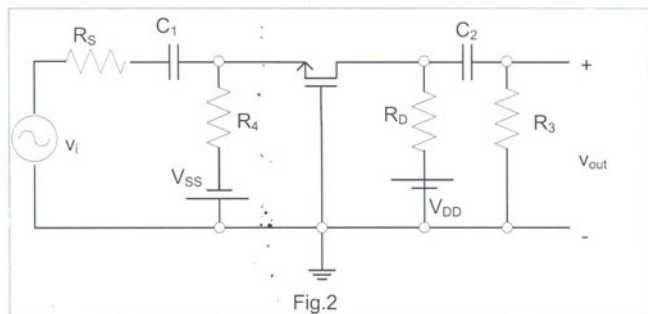




Total Marks: - 70


Question 1: (20 marks)


- (a) Draw the low frequency and mid-band small signal model for the shown amplifier in Fig.1 if $R_S = 100\Omega$, $R_1 = 1.3K\Omega$, $R_D = 4.3K\Omega$, $R_3 = 100K\Omega$, $C_1 = 4.7\mu F$, $C_2 = 1\mu F$ and $g_m = 5mA/V$. (7 marks)
- (b) Drive the expression of the mid-band gain and the low frequency gain of the amplifier. Assume $r_{ds} = \infty$. (7 marks)
- (c) What are the lower-cut off frequency (using short-circuit time constant method)? (6 marks)



Solution:

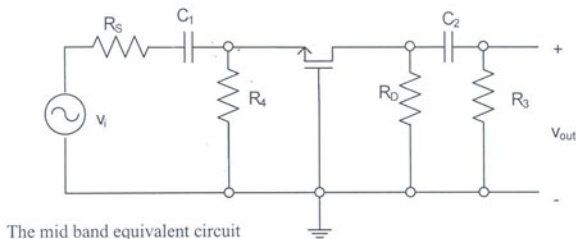- (a) The low frequency equivalent circuit



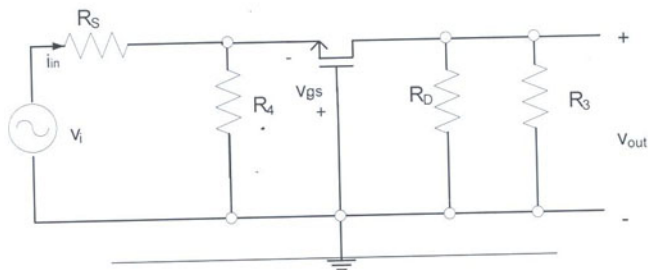

(b) The mid band frequency gain

$$v_{out} = -g_m v_{gs} (R_3 // R_D)$$

$$v_{gs} = v_g - v_s = 0 - v_s = -v_s$$

$$v_s = v_{in} - i_{in} R_S$$

$$i_{in} = -g_m v_{gs} - \frac{v_{gs}}{R_4} = -v_{gs} \left(g_m + \frac{1}{R_4} \right)$$

$$\therefore v_{gs} = -(v_{in} - i_{in} R_S) = -v_{in} - v_{gs} R_S \left(g_m + \frac{1}{R_4} \right)$$

$$v_{gs} = \frac{-v_{in}}{1 + R_S \left(g_m + \frac{1}{R_4} \right)}$$

$$\therefore A_{MF} = \frac{v_{out}}{v_{in}} = \frac{+g_m (R_3 // R_D)}{1 + R_S \left(g_m + \frac{1}{R_4} \right)} = 13.06$$


(c) The voltage gain of the amplifier

$$A_{LF} = \frac{A_{MF} \times S^2}{(S + w_{LC1})(S + w_{LC2})}$$

We have two zeros at $S = 0$: ($w = 0$)


The poles are generated due to the presence of the external capacitors; to get the poles locations we will use the short circuit time constant method;

The pole generated from C1

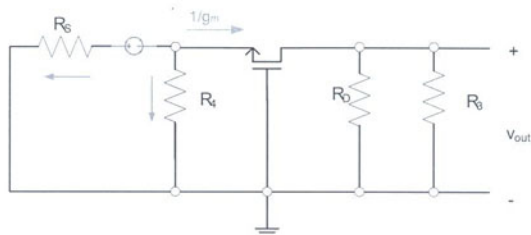

$$\omega_{LC1} = \frac{1}{C_1 R} = \frac{1}{C_1 \left(R_5 + \left(R_4 // \frac{1}{g_m} \right) \right)}$$

(d) The pole generated from C2

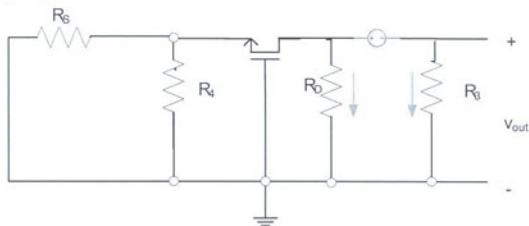

$$\omega_{LC2} = \frac{1}{C_2 R} = \frac{1}{C_2 (R_D + R_3)}$$

$$f_{LC1} = \frac{1}{2\pi C_1 \left(R_5 + \left(R_4 // \frac{1}{g_m} \right) \right)} = 123.8 \text{ Hz}$$

$$f_{LC2} = \frac{1}{2\pi C_2 (R_D + R_3)} = 1.526 \text{ Hz}$$

The overall lower cut-off frequency

$$f_i = \sqrt{f_{LC1}^2 + f_{LC2}^2} = 123.81 \text{ Hz}$$

Question 2: (15 marks)

Consider the cascode circuit in Fig.2 with the following components, $R_s = 4 \text{ k}\Omega$, $R_1 = 18 \text{ k}\Omega$, $R_2 = 4 \text{ k}\Omega$, $R_E = 3.3 \text{ k}\Omega$, $R_C = 6 \text{ k}\Omega$, $V_{CC} = 15 \text{ V}$, $r_\pi = 1000\Omega$. Assume that Q_1 and Q_2 are of the same type so $I_E = 1\text{mA}$, $\beta = 100$, $C_{bc} = 1 \text{ pF}$, $C_{be} = 13.9 \text{ pF}$, and neglect r_o . Calculate the mid band gain $A_{\text{mid-band}}$, the high frequency gain A_H and by using open-circuit time constant method calculate f_H .


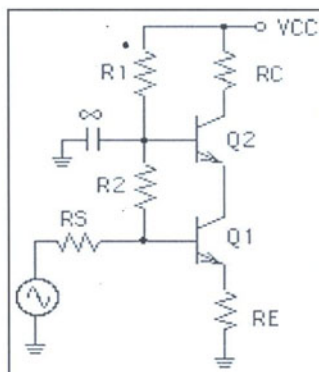


Fig.2


Solution:

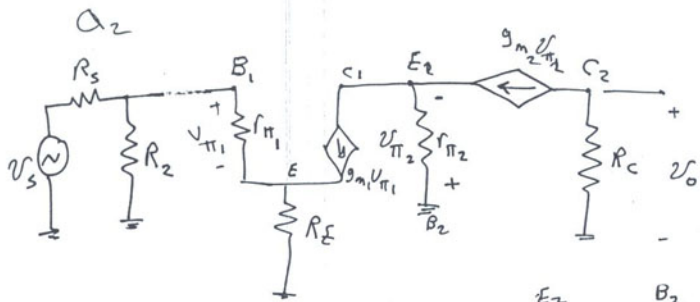

* $V_o = -g_{m1} V_{\pi 2} R_C$

* $V_{\pi 2} = g_{m1} V_{\pi 1} \frac{1}{g_{m2}}$

* $V_{\pi 1} = i_{b1} r_{\pi 1}$

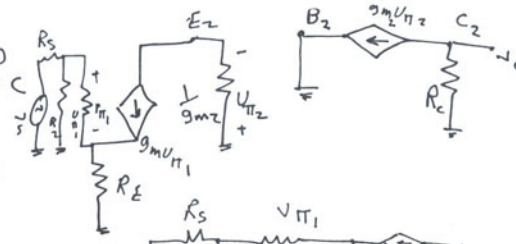

mesh eq.

$V_x = i_{b1} (R_x + r_{\pi 1} + R_E) + R_E \beta i_{b1}$


$V_x = i_{b1} [R_x + r_{\pi 1} + R_E (\beta + 1)]$

$V_{\pi 1} = \frac{V_x r_{\pi 1}}{R_x + r_{\pi 1} + R_E (\beta + 1)}$




$V_{\pi 1} = V_s \frac{(r_{\pi 1} \parallel (\beta + 1) R_E)}{(r_{\pi 1} \parallel (\beta + 1) R_E) + (R_2 \parallel R_S)}$

$A_v = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{\pi 2}} * \frac{V_{\pi 2}}{V_1} * \frac{V_{\pi 1}}{V_s} =$

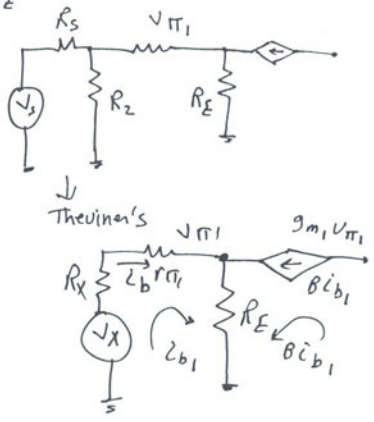$A_v = -g_m R_C \frac{[r_{\pi 1} \parallel (\beta + 1) R_E]}{[(r_{\pi 1} \parallel (\beta + 1) R_E) + (R_2 \parallel R_S)]}$



* high frequency response so

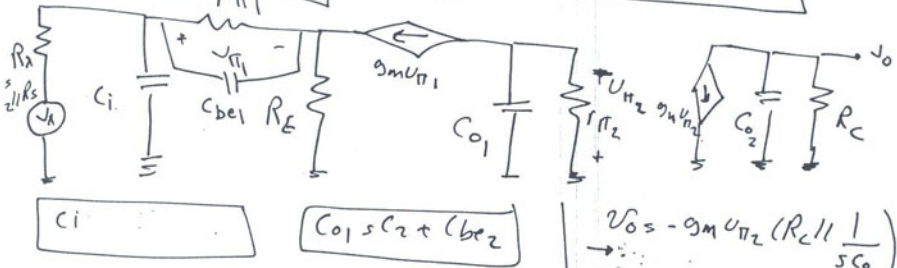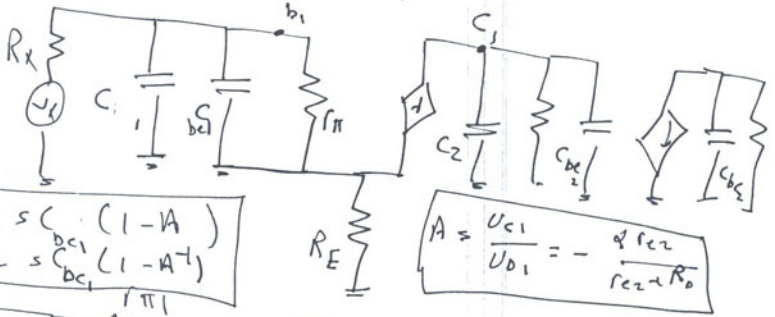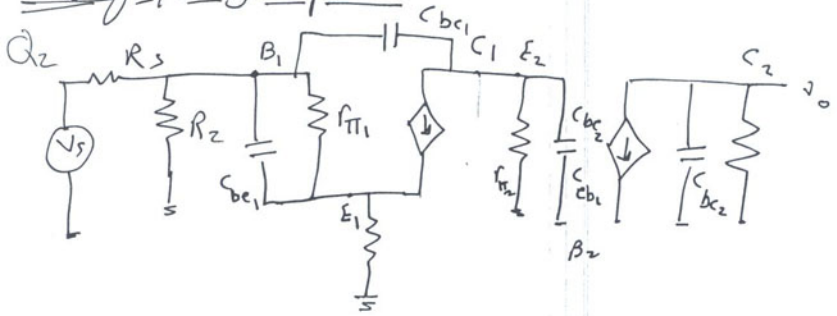


$A_{H1} =$

$$f_H = \frac{1}{\sqrt{\left(\frac{1}{f_{HCr}}\right)^2 + \left(\frac{1}{f_{HCo1}}\right)^2 + \left(\frac{1}{f_{HCo}}\right)^2}}$$

$V_{O1} = -g_m U_{\pi 2} (R_L \parallel \frac{1}{sC_0})$
 $\rightarrow \therefore V_{\pi 2} = \dots g_m U_{\pi 1} Z$

$Z \approx r_{\pi 2} \parallel \frac{1}{sC_1}$
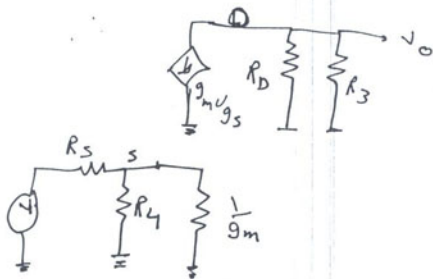
$$Q_2 \quad E \quad \frac{1}{g_m} \quad B$$



$$A_{\text{Mid-band}} = \frac{\beta^2 [R_2 \parallel [(\beta+1)(r_e + R_E)]] * R_C}{(\beta+1)^2 (R_E + r_e) [R_S + R_2 \parallel [(\beta+1)(r_e + R_E)]]}$$

$$= \frac{g_m^2 r_e r_{e1} [R_2 \parallel (\beta+1)(r_e + R_E)]}{(R_E + r_{e1}) [R_S + R_2 \parallel [(\beta+1)(R_E + r_e)]]}$$

$$A_{H1}(s) \rightarrow A_{\text{Mid-band}} \frac{1}{(1 + s C_{bc} R_C) (1 + s C_{c1} (R_S \parallel R_2)) (1 + s g_m r_e) (1 + s [C_{bc} \left(\frac{(R_S \parallel R_2)}{(\beta+1)} + R_E \right) \parallel r_e])}$$

Question 3: (20 marks)

- a) For the feedback amplifier shown in the figure Fig.3, drive expressions for A , β , A_f , R_{in_f} , R_{of} . Neglect r_{ds} and the body effect, $g_{m1} = g_{m2} = 5\text{mA/V}$, $R_D = 10\text{K}\Omega$, $R_i = 10\text{K}\Omega$ and $R_f = 10\text{K}\Omega$. (2 marks per one)


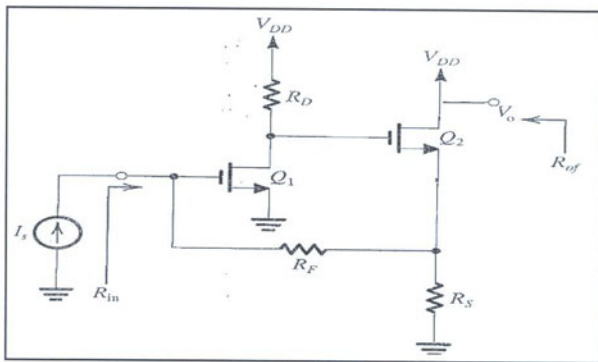
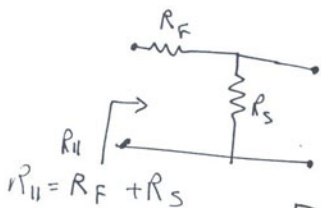


Fig.3

Solution:


Q3

a] shunt-series \rightarrow (1 mark)

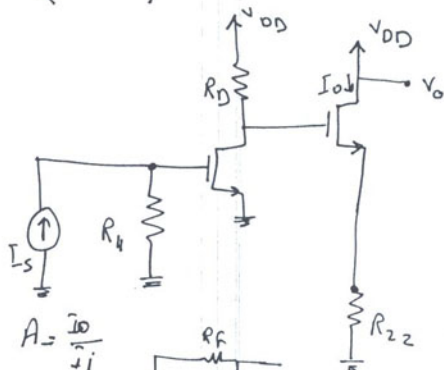


$$R_{i1} = R_F + R_S$$

$$A = \frac{I_o}{I_i}$$

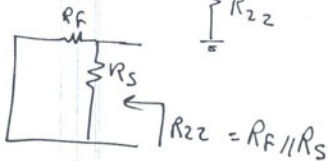

$$R_{z2} = R_F \parallel R_S$$

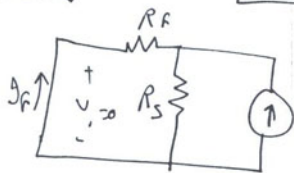

$$I_o = \beta_s \frac{I_F}{I_o}$$

$$\beta = \frac{-R_S}{R_F + R_S}$$

$$R_{of} = (1 + A\beta) R_o$$

$$R_{if} = \frac{R_i}{(1 + A\beta)}$$

$$A_f = \frac{A_F}{1 + A\beta}$$

$$A = \frac{I_o}{I_s} = \frac{-g_m R_o (R_F + R_S)}{\frac{1}{g_m} + R_F \parallel R_S}$$

$$R_i = R_F + R_S$$

$$R_o = \frac{1}{g_m} + R_F \parallel R_S$$

b) Let the output of Q2 be taken as the voltage at the source of Q2 as shown in the figure Fig.4. Find the expressions for A , β , A_{fs} , R_{infs} , R_{of} . Neglect r_{ds} and the body effect, $g_{m1} = g_{m2} = 5\text{mA/V}$, $R_D = 10\text{K}\Omega$, $R_S = 10\text{K}\Omega$ and $R_F = 10\text{K}\Omega$. (2 marks per one)


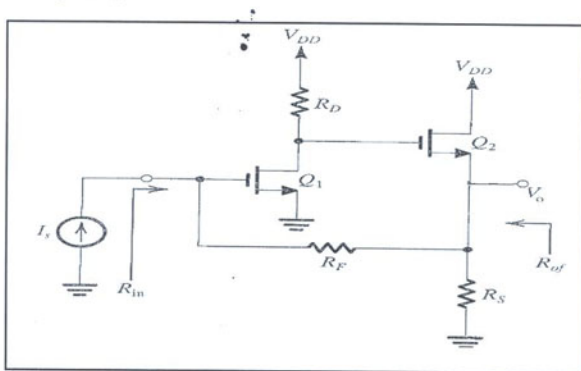
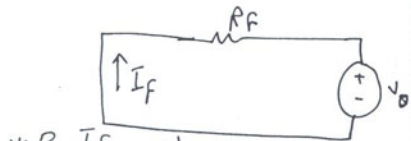


Fig.4

Solution:

Q3 [b] shunt-shunt \rightarrow (1 mark)

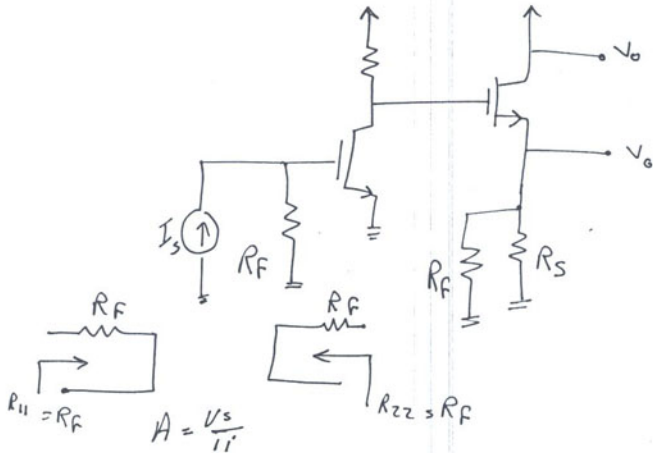

$$*B = \frac{I_f}{V_o} = -\frac{1}{R_F} A_f = -\frac{A}{1+A\beta}$$

$$R_{if} = \frac{R_i}{(1+A\beta)} \Rightarrow R_i = R_F$$

$$R_{of} = \frac{R_o}{(1+A\beta)} \Rightarrow R_o, R_F \parallel R_S \parallel \frac{1}{g_m}$$

$$A = \frac{-g_m R_o R_F (R_F \parallel R_S)}{\frac{1}{g_m} + R_F \parallel R_S}$$

Question 4: (15 marks)

A two stage feedback circuit is shown in the figure Fig.5. Assume that both transistors are identical and have a $\beta = 100$, $r_{\pi} = 1000\Omega$, $R_C = 2\text{ K}\Omega$, $R_1 = 5\text{ K}\Omega$, $R_C = 10\text{ K}\Omega$, $V_{CC} = 15\text{ V}$, and neglect r_o . Use the method of feedback analysis to find A , β , A_{fs} , R_{infs} , R_{of} . (3 marks per one)

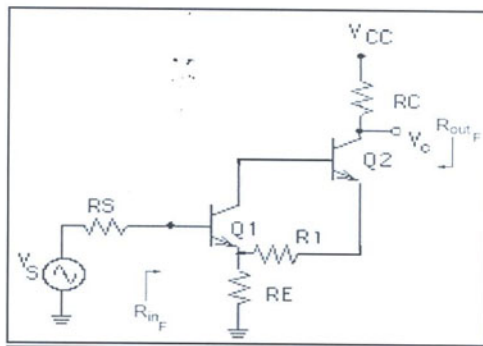


Fig.5

Solution:


Q4 series-series (1 mark)

$$A = \frac{I_o}{V_s}$$

$$A_f = \frac{I_o}{V_s} = \frac{A}{1+AB}$$

$$R_{if} = R_i(1+AB)$$

$$R_{of} = (1+AB)R_o$$

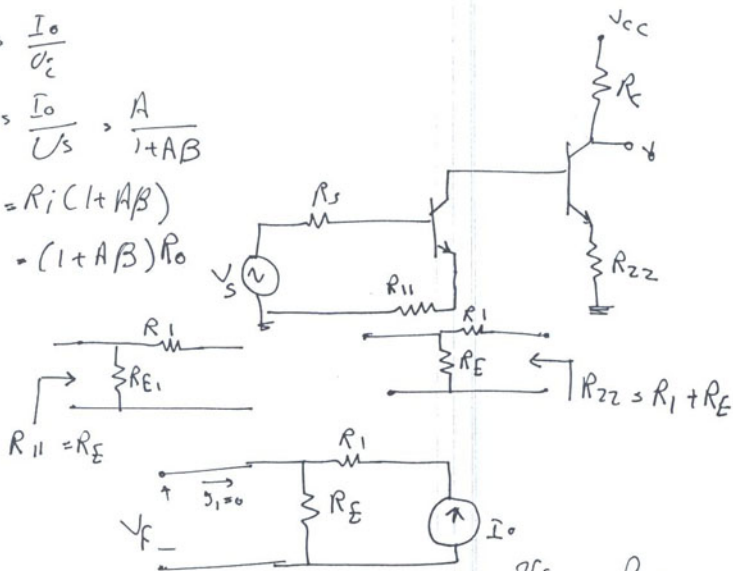

$$R_i = (\beta+1)(r_e + R_E)$$

$$R_o = R_E + R_1 + r_e$$

$$A = \frac{1}{R_s + r_e + R_E}$$