
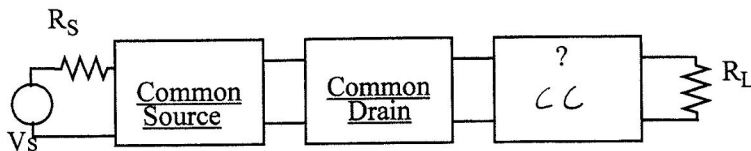


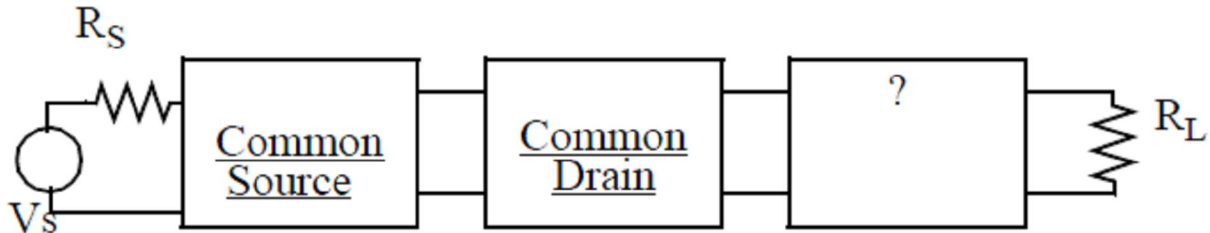


The following multistage amplifier is meant to deliver a voltage signal to a relatively small ohmic load of $1K\Omega$. Mark your choice of the last stage, and write a brief justification.




A CC has very low output resistance (less than a CD) and a high input resistance. It makes a good final stage voltage buffer

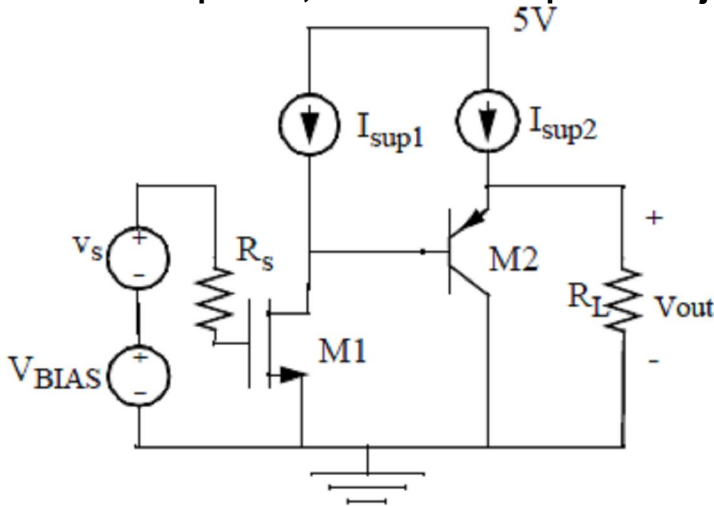The following is a two stage voltage amplifier employing a n-channel CS stage, and a pnp CC stage. Note that there are no numerical substitutions or calculations in parts a, b and c of this problem - just symbolic expressions!



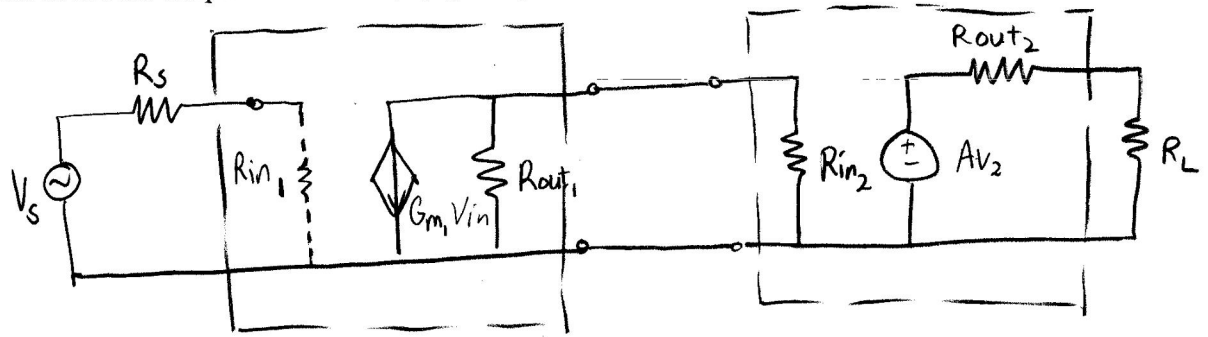a) Draw the small signal model for this two stage voltage amplifier.

(OK to use the simplified formulae). (6 points)



b) Derive the *expressions* for the quantities shown below, in terms of the device parameters (OK to use the simplified formulae).

- a. R_{in1} , R_{out1} for the first stage.
- b. R_{in2} , R_{out2} and A_{v2} for the second stage.

Parameter	Expression
G_{m1}	g_{m1}
R_{in1}	∞
R_{out1}	$r_{o1} \parallel r_{oc1}$
A_{v2}	1
R_{in2}	$r_{\pi} + \beta_0 (r_{o2} \parallel r_{oc2} \parallel R_L)$
R_{out2}	$\frac{1}{g_{m2}} + \frac{R_{out1}}{\beta_0}$

- a) Derive *expressions* for the A_v , R_{in} , R_{out} , as well as v_{out} / v_s in terms of the device parameters.
- b) Assume that $V_{BIAS} = 1.5V$, and that the minimum voltage across the current sources is $0.5V$. Find the maximum and minimum voltages at the drain of M1 and at the emitter of M2. Make sure you mention the limiting reason for each case (i.e. transistor X falls out of saturation, or current source Y hits its minimum voltage drop, etc.)


- $V_{dmin} = V_{GS} - V_T = 1.5V - 1V = 0.5V \therefore V_{emin} = 0.5V + 0.7V = 1.2V$
- $V_{dmax} \neq 4.5V$ because $V_e = 4.5V + 0.7V = 5.2V > V_{DD}$
 $V_{emax} = 4.5V \therefore V_{dmax} = 4.5V - 0.7V = 3.8V$

Node	Min Voltage	Reason for Min Voltage	Max Voltage	Reason for Max Voltage
drain of M1	0.5V	V_{psat} of M1	3.8V	Min voltage across I_{SUP2} & V_{EB} of M2
emitter of M2	1.2V	V_{dsat} of M1 & V_{EB} of M2	4.5V	Min voltage across I_{SUP2}

FB amplifier

PARAMETERS:

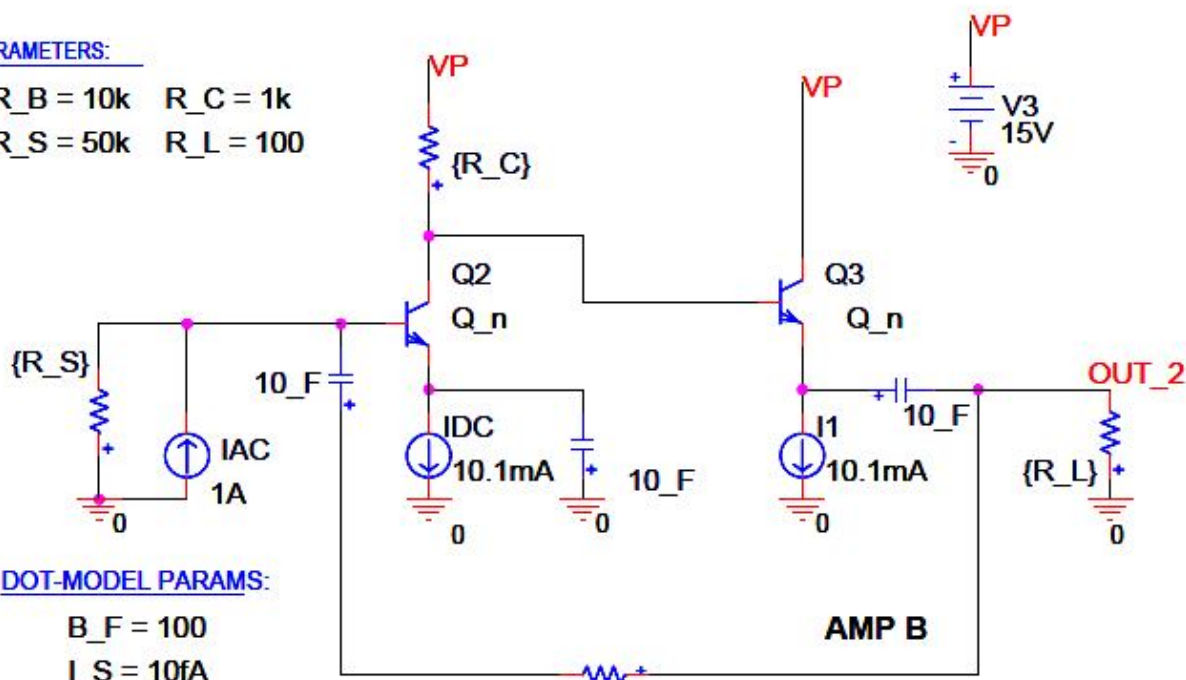$R_B = 10k$ $R_C = 1k$
 $R_S = 50k$ $R_L = 100$



DOT-MODEL PARAMS:

$B_F = 100$
 $I_S = 10fA$

.model Q_n NPN (Bf={B_F} Is={I_S}) {R_B}


For the shown FB Amplifier,

1. Identify the topology of the FB. what kind of amplifier (V/V, A/A etc.) is Amp A? Amp B? Explain in your outline


Answer: Both amplifiers are transresistance amplifiers.

Outline: Both amplifiers can be arranged as shown in Figure 2, so both are shunt-shunt FB amps → current input and voltage output or transresistance gain.

2. Find the feedback parameter β_{FB} .

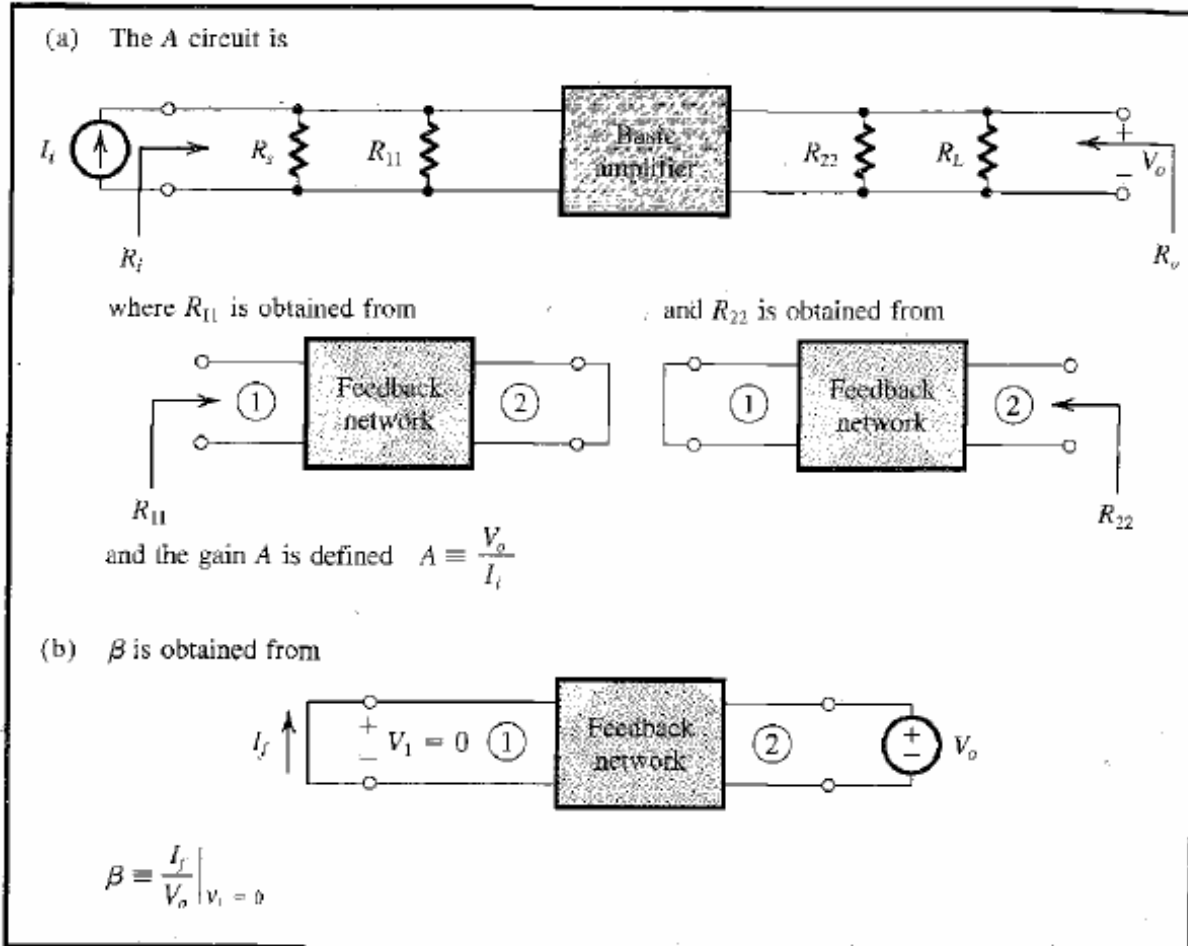

3. Draw the amplifier without FB.

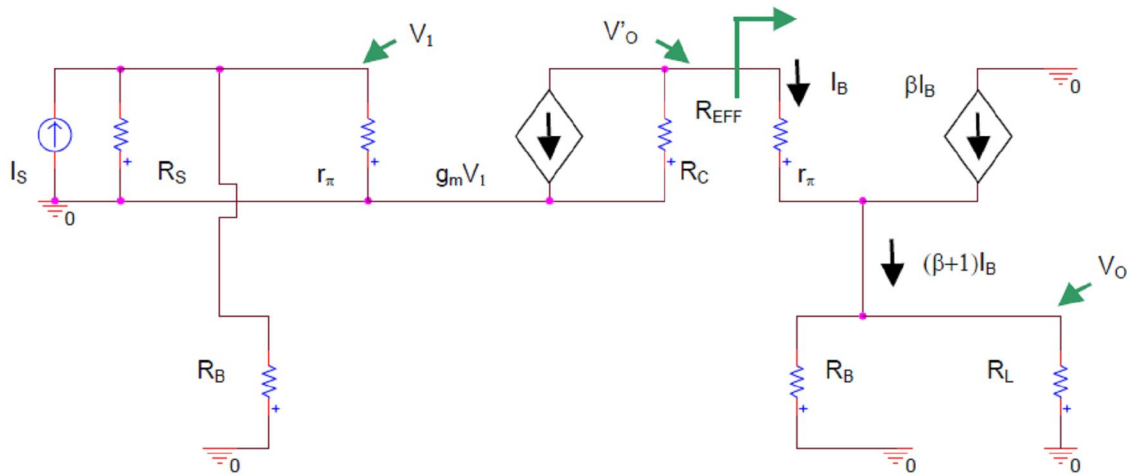

4. Find gain, input resistance and output resistance without FB.

$$PF_B = 1 + \beta_{FB} A_{LB} = 1 + \frac{1}{R_B} g_m (R_C // R_{EFF}) (R_S // R_B // r_\pi)$$

$$R_{EFF} = r_\pi + (\beta + 1)(R_B // R_L).$$

EQ. 6

$$\frac{V'_O}{I_S} = -g_m (R_C // R_{EFF}) (R_S // R_B // r_\pi).$$

The gain V_O/V'_O is just the gain of the VF, which is nearly unity. More exactly,

EQ. 7

$$\frac{V_O}{V'_O} = \frac{R_L // R_B}{R_L // R_B + r_E} \approx 1.$$

Hence, provided $R_L // R_B \gg r_E$, we can use EQ. 6 as the gain of Amp B. That is,

EQ. 8

$$\frac{V_O}{I_S} = \frac{V'_O}{I_S} \frac{V_O}{V'_O} \approx -g_m (R_C // R_{EFF}) (R_S // R_B // r_\pi)$$

With this approximation the PF for Amp B is

EQ. 9

$$PF_B = 1 + \beta_{FB} A_{LB} = 1 + \frac{1}{R_B} g_m (R_C // R_{EFF}) (R_S // R_B // r_\pi),$$

with A_{LB} = loaded gain for Amp B, namely, $A_{LB} = -g_m (R_C // R_{EFF}) (R_S // R_B // r_\pi)$.

5. Find the voltage gain, input resistance and output resistance of the shown FB Amplifier. Hint: neglect r_o

A_L/PF

Question 3 [Power Amplifiers]:- Consider the output stage shown in Fig. 5. The BJT has $\beta = \infty$ and initially assume that $V_{BE} = 0.7$ V when it is on.

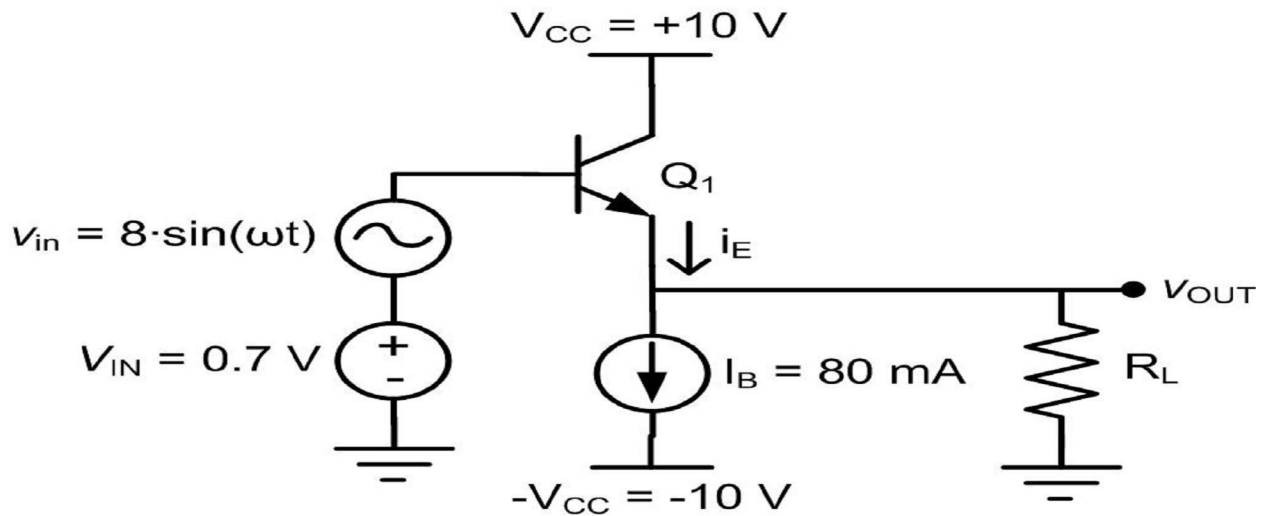


Figure 5: BJT output stage.

- a) Choose R_L so that 0.32 W of power is dissipated in the load under the given input conditions.
 b) What class of operation is the output stage in under this condition?

(a) For voltage follower, $V_{out} = V_{in} = 8 \cdot \sin \omega t$.

$$\therefore P_L = \left(\frac{8}{\sqrt{2}}\right)^2 \cdot \frac{1}{R_L} = 0.32 \Rightarrow R_L = \frac{64}{2 \cdot 0.32} = 100 \Omega$$

(b) When $V_{out} = -8 \text{ V}$, $I_{EL} = \frac{8}{100} = 80 \text{ mA}$, supplied by I_B

\therefore class A.

(c) See plot.

$$(d) P_S = 20 \cdot 80 \text{ E-}3 = 1.6 \text{ W}$$

$$\therefore \eta = \frac{P_L}{P_S} = \frac{0.32}{1.6} = 20\%$$

- c) What is the conversion efficiency of the output stage under these conditions?

$$\eta_{C \%} = \frac{P_{av}}{P_{DC}} * 100 = \frac{\frac{1}{2} \frac{V_m^2}{R_L}}{2 V_{CC} I} * 100 = 25 \frac{V_m^2}{V_{CC} (I R_L)}$$

$$V_{m, \max} = V_{CC} \quad R_{L, \min} = \frac{(V_{CC} - V_{CE2, \text{sat}})}{I} \cong \frac{V_{CC}}{I}$$

$$I R_{L, \min} = V_{CC}$$

$$\eta_{C, \max \%} = 25$$

- d) Find the maximum conversion efficiency.

(i) If R_L is large: $I > i_L$

$$-V_{CC} + v_{CE2sat} = v_{o\min}$$

$$I > i_L$$

$$I > v_{o\min}/R_L$$

$$I \geq \frac{|-V_{CC} + V_{CE2sat}|}{R_L}$$

$$IR_L > (V_{CC} - V_{CE2,sat}) \quad R_L > \frac{(V_{CC} - V_{CE2,sat})}{I}$$

$$R_{L, \min} = \frac{(V_{CC} - V_{CE2,sat})}{I}$$

a) Find the maximum power delivered to the load

(b) The power delivered to the load

$$P_{av} = \frac{1}{2} V_m I_m = \frac{1}{2} \frac{V_m^2}{R_L}$$

The maximum power delivered to the load

$$V_{m, \max} = V_{CC} \quad V_{\min} = -V_{CC} + V_{CE2,sat} \quad \left| \text{when } Q_2 \text{ is sat.} \right. \cong -V_{CC}$$

$$P_{av, \max} = \frac{1}{2} \frac{V_{CC}^2}{R_L} \quad V_{\max} = V_{CC} - V_{CE1,sat} \quad \left| \text{when } Q_1 \text{ is sat.} \right. \cong V_{CC}$$

e) Plot v_{out} and i_E in the space provided in **Fig. 2**.

PROBLEM 5 (cont'd)


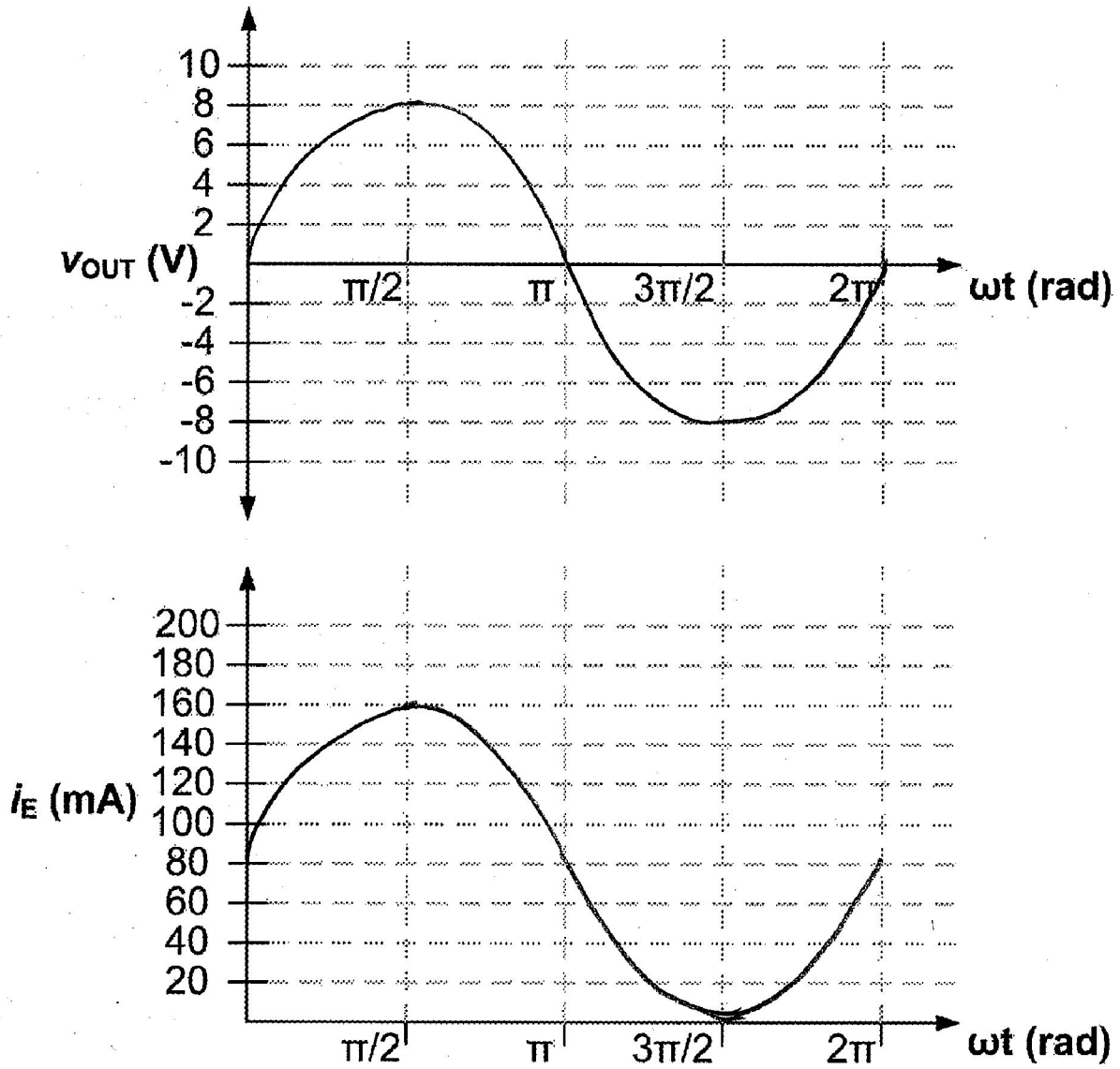


Figure 6: Power amplifier output voltage and emitter current.

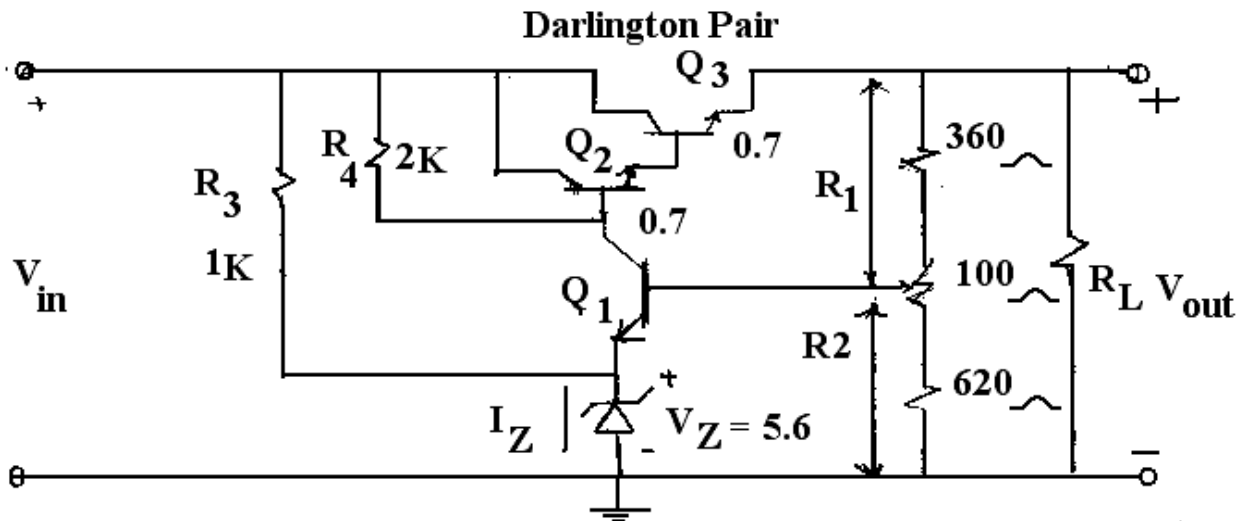Question 4 [Voltage Regulator]:-

For the following Voltage Regulator shown in the Figure,



For the following Voltage Regulator shown in **Fig. 5**,

- What are the minimum and maximum output voltages in the above circuit?
- If $V_{out} = 10\text{ V}$, $R_L = 5\ \Omega$, β_1 (for Q_1) = $\beta_2 = 100$, $\beta_3 = 50$ and $V_{in} = 20\text{ V}$, what is the current through the Zener diode?
- Calculate the power dissipation of the Q_3 for a load voltage of 10 V and a load current of 2 A when $V_{in} = 20\text{ V}$

[1] What are the minimum and maximum output voltages in the above circuit?

$$\therefore V_{out} = \frac{1}{\beta} (V_Z + V_{BE1})$$

$$\text{where } \beta = \frac{R_2}{R_1 + R_2} \Rightarrow \frac{A_f}{f} = \frac{1}{\beta} = 1 + \frac{R_1}{R_2}$$

$$\therefore \frac{A_f}{f}_{\text{Max}} = 1 + \frac{360 + 100}{620} = 1.74$$

and

$$A_{f_{\min}} = 1 + \frac{360}{620 + 100} = 1.5$$

$$\therefore V_{\text{out Max}} = 1.74 (5.6 + 0.7) \cong 11 \text{ V}$$

$$V_{\text{out Min}} = 1.5 (5.6 + 0.7) = 9.45 \text{ V}$$

[2] if $V_{\text{out}} = 10 \text{ V}$, $R_L = 5 \Omega$, $\beta_1 = \beta_2 = 100$

$\beta_3 = 50$ and $V_{\text{in}} = 20 \text{ V}$

What is the current through the Zener diode?

$$I_Z = I_{R_3} + I_{C_1} \quad \text{①}$$

where $I_{R_3} = \frac{V_{\text{in}} - V_Z}{R_3} = \frac{20 - 5.6}{1\text{k}} = 14.4 \text{ mA}$

[2] if $V_{out} = 10V$, $R_L = 5\Omega$, $\beta_1 = \beta_2 = 100$

$\beta_3 = 50$ and $V_{in} = 20V$

What is the current through the Zener diode?

$$I_Z = I_{R_3} + I_{C_1} \quad (1)$$

where
$$I_{R_3} = \frac{V_{in} - V_Z}{R_3} = \frac{20 - 5.6}{1K} = 14.4 \text{ mA}$$

and

$$I_{C_1} = I_{R_4} - I_{\beta_2} \quad (2)$$

where
$$I_{R_4} = \frac{V_{in} - V_{\beta_2}}{R_4} = \frac{20 - [0.7 + 0.7 + 10]}{2}$$

$$I_{R_4} = 4.3 \text{ mA}$$

and

$$I_{\beta_2} = \frac{I_{C_2}}{\beta_2} = \frac{1}{\beta_2} \frac{I_{C_3}}{\beta_3} \cong \frac{1}{\beta_2 \beta_3} I_L$$

and

$$I_{\beta_2} = \frac{I_{C_2}}{\beta_2} = \frac{1}{\beta_2} \frac{I_{C_3}}{\beta_3} \approx \frac{1}{\beta_2 \beta_3} I_L$$

where

$$I_L = \frac{V_{out}}{R_L} = \frac{10V}{5\Omega} = 2A$$

$$\therefore I_{\beta_2} = \frac{2 \times 1000}{100 \times 50} = 0.4 \text{ mA}$$

From (2)

$$\therefore I_{C_1} = 4.3 - 0.4 = 3.9 \text{ mA}$$

and

From (2)

$$\therefore I_{C_1} = 4.3 - 0.4 = 3.9 \text{ mA}$$

and
from (1)

$$I_2 = 14.4 + 3.9 = \underline{\underline{18.3 \text{ mA}}}$$

(4)

[3] Calculate the power dissipation of the Q_3 for

a load Voltage of 10V and a load Current of 2A

When $V_{in} = 20V$

$$P_{D_{Q_3}} = V_{CE_3} I_{C_3}$$

$$P_{D_{Q_3}} = V_{CE_3} I_{C_3}$$
$$= (V_{in} - V_{out}) (I_L)$$

$$P_{D_{Q_3}} = (20 - 10) (2) = 20 W \quad * \checkmark !!$$