

4th year (Communication)
Subject: Electronics (4-A)

1- ch 5 - P160 (CMOS Digital Integrated Circuits)
(Sung-Mok Kang & Yusuf Leblebici)

2

(V_{OL}) M_1 is Linear

$$\frac{K_n}{2} \left(2V_{DD} - V_{To} \right) V_{OL} - V_{OL}^2 = \frac{V_{DD} - V_{O/P}}{R_L}$$

$$V_{OL} = V_{DD} - V_{To} + \frac{1}{K_n R_L} - \sqrt{\left(V_{DD} - V_{To} + \frac{1}{K_n R_L} \right)^2 - \frac{2V_{DD}}{K_n R_L}}$$

$$V_{OL} = 5 - 0.9 + \frac{1}{50 \times 10^6 \times 150 \times 10^3} - \sqrt{17 - 9211 - 1.333}$$

$$= 4.2332 - 4.0728 = 0.1605V$$

V_{OH} M_1 is cut off


$$IR = 0 \quad \therefore \frac{V_{DD} - V_O}{R_L} = 0 \quad V_O = V_{OH} = V_{DD} = 5V$$

$V_{IH} \Rightarrow M_1$ is linear

$$\frac{V_{DD} - V_O}{R_L} = \frac{K_n}{2} \left(2(V_{IH} - V_{To}) V_O - V_O^2 \right)$$

$$V_{IH} = V_{To} + \sqrt{\frac{8}{3} \frac{V_{DD}}{K_n R_L}} - \frac{1}{K_n R_L} = 2.1V$$

$V_{IL} \Rightarrow M_1$ is sat.

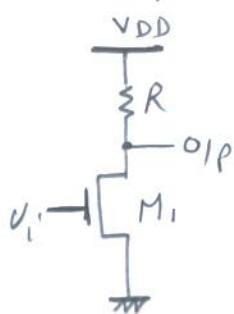





2

$$\frac{V_{DD} - V_o}{R_L} = \frac{k_n}{2} (V_{IL} - V_{To})^2$$

$$\frac{k_n}{2} 2(V_{IL} - V_{To}) = \frac{1}{R_L} \quad V_{oL} = \frac{1}{k_n R_L} + V_{To} = 1.0333V$$

$$NM_L = V_{IL} - V_{oL} = 1.033 - 0.16053 = 0.87277$$
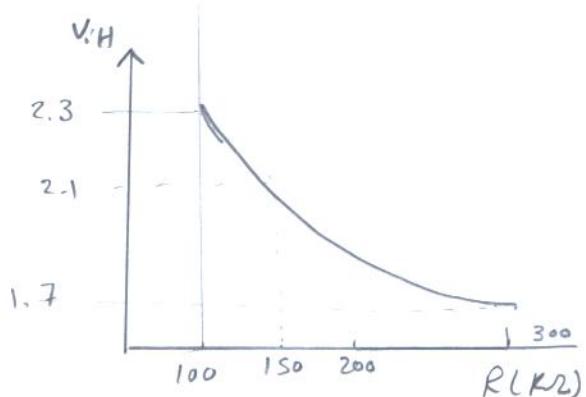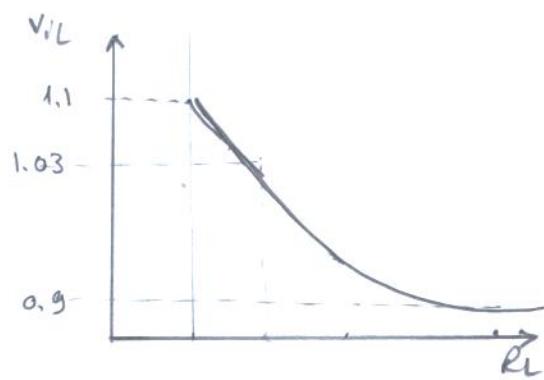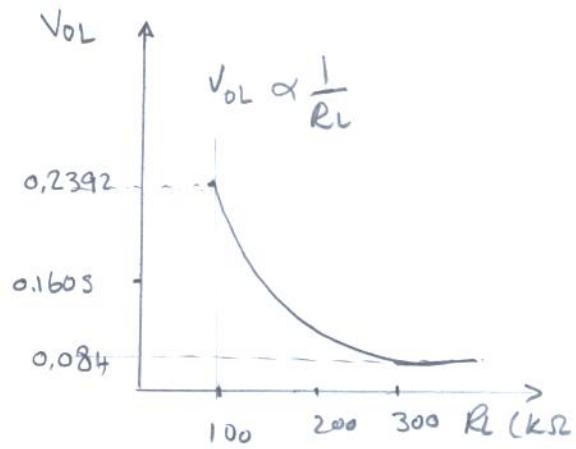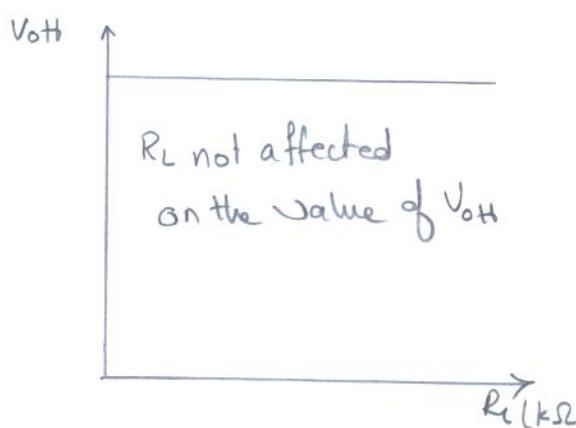
$$NM_H = V_{oH} - V_{IH} = 5 - 2.1 = 2.9$$



(2)

4-

$$V_{DD} = 5V$$

(ii) average Current method

$$\tau_{fall} = \frac{\Delta V_{CL}}{I_{avg\ fall}}$$

$$I_{avg\ fall} = \frac{k_n}{4} \left[(V_{DD} - V_{T0})^2 + (2(V_{DD} - V_{T0})V_{OL} - V_{OL}^2) \right]$$

$$= \frac{200 \times 10^{-6}}{4} \left[16 + (2 \times 4 \times 0.5 - 0.5^2) \right] = 9.875 \times 10^{-4}$$

$$\tau_{fall} = \frac{(4.5 - 0.5) \times 10^{-12}}{9.875 \times 10^{-4}} = 4.05 \text{ ns}$$

Using diff. equ.

$$\tau_{fall} = -\frac{C_L}{k_n/2} \int_{V_{OLi.}}^{V_{DD}-V_T} \frac{dV_O}{(V_{DD}-V_{T0})^2} = -\frac{2C_L}{k_n(V_{DD}-V_{T0})^2} * \frac{(V_{DD}-V_{T0} - V_{OLi.})}{1}$$

$$= 0.3125 \text{ ns}$$


$$\tau_{delay} = -\frac{2C_L}{k_n} \int_{V_{DD}-V_T}^{V_{OLf.}} \frac{dV_O}{(2(V_{DD}-V_{T0})V_O - V_O^2)}$$

$$= \frac{C_L}{k_n(V_{DD}-V_{T0})} * \ln \left[\frac{2(V_{DD}-V_{T0})}{V_{OLf.}} - 1 \right] =$$

$$= 3.385 \text{ ns}$$


b

$$\frac{W}{L} =$$

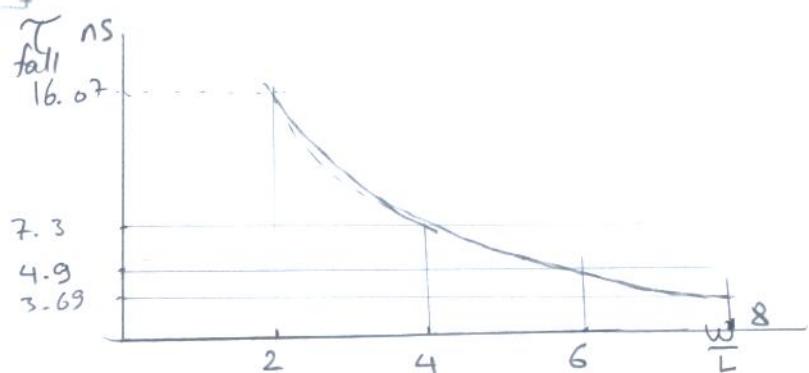

$$\therefore T_{fall} \propto \frac{1}{\mu_n C_{ox}}$$

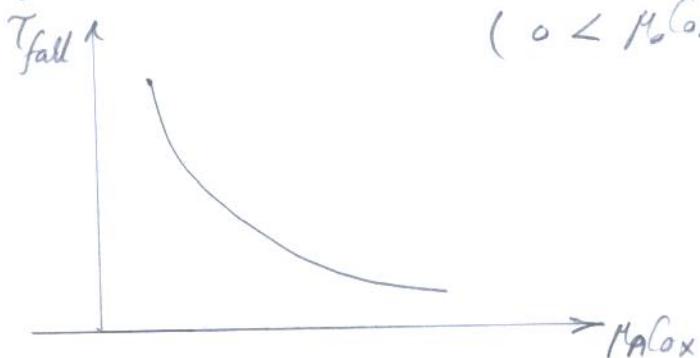So as T_{fall} increase $\mu_n C_{ox}$ decrease
 $(0 < \mu_n C_{ox} \leq 25 \mu A/V^2)$



3. chapter 6. p. 197

5. chapter 7 p. 260

6.

A	B	O/P
0	0	1
0	1	0
1	0	0
1	1	0

$$(\forall_{0H} \quad V_A = V_B = 0)$$

$$\frac{K_L}{2} \left(-V_{T_L}(V_0)(V_{DD} - V_0) - (V_{DD} - V_0)^2 \right) = 0$$

$$V_0 = V_{0H} = V_{DD} = 5V$$

$$V_{oL} \rightarrow A=0, B=1$$

$$\frac{K_L}{2} (-V_{T_L}(V_0))^2 = \frac{K_n}{2} (2(V_{DD} - V_{T_0})V_{oL} - V_{oL}^2)$$

$$V_{oL} = V_{DD} - V_{T_0} - \sqrt{(V_{DD} - V_{T_0})^2 - \frac{K_L}{K_B} (V_{T_L}(V_0))^2}$$

$$\begin{aligned} V_{T_L} &= V_{T_{oL}} - 8 \left(\sqrt{12\phi_F + V_{oL}} - \sqrt{12\phi_F} \right) \\ &= -3 - 0.4 * 0.14214 = -2.95V \end{aligned}$$

$$V_{oL} = 0.0917V$$


$$V_{oL} \Rightarrow A=1, B=0$$

$$\begin{aligned} V_{oL} &= V_{DD} - V_{T_0} - \sqrt{(V_{DD} - V_{T_0})^2 - \frac{k_L}{k_A} (V_{T_L}(V_o))^2} \\ &= 0.1856 \text{ V} \end{aligned}$$

$$V_{oL} \Rightarrow A=1, B=1$$

$$\frac{k_L}{2} (1 - V_{T_L}(V_o))^2 = \frac{k_A}{2} (2(V_{DD} - V_{T_0})V_{oL} - V_{oL}^2) + \frac{k_B}{2} (2(V_{DD} - V_{T_0})V_{oL} - V_{oL}^2)$$

$$V_{oL} = 0.04558 \text{ V}$$

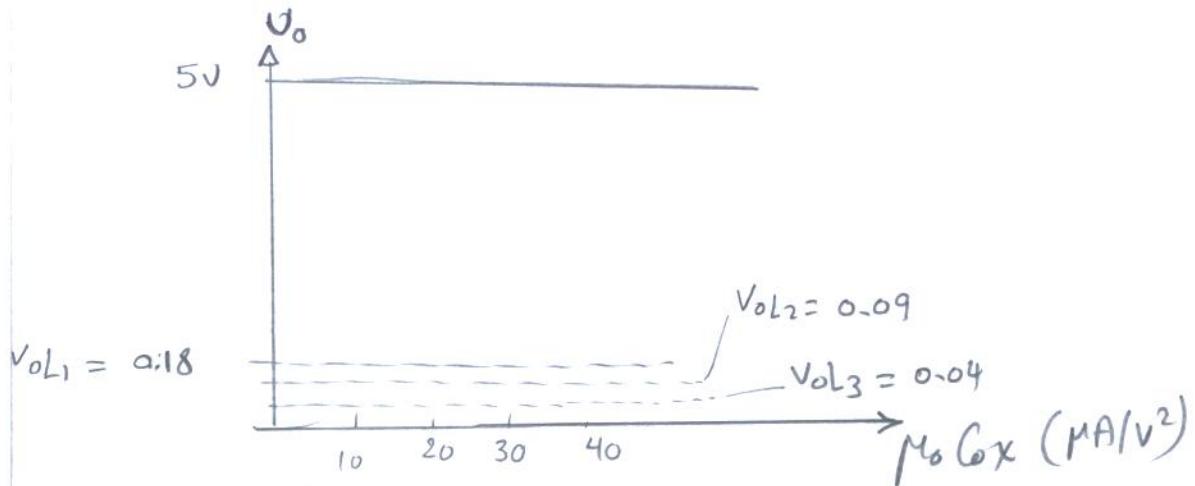

7 chapter 8 p 320