

Power


①

$$V_g = 13800 \text{ V } \angle 0^\circ$$


$$Z_g = 0.009 + 0.9j \text{ } \Omega/\text{ph}$$

$$Z_{T.L} = 0.02 + 0.18j \text{ } \Omega/\text{ph}$$
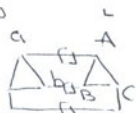
$$Z_{\text{load}} = 7.056 + 3.417j \text{ } \Omega/\text{ph}$$



② for single phase eq. circuit

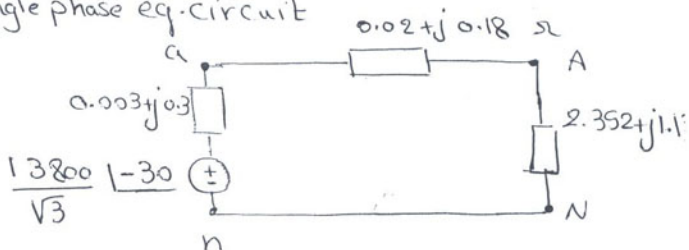

$$\begin{aligned} \text{③ } I_{aA} &= \frac{\frac{13800}{\sqrt{3}} \angle -30^\circ}{2.375 + j1.619} = \frac{13800 \angle -30^\circ}{\sqrt{3} \cdot 2.87 \angle 34.28^\circ} \\ &= 2776.1 \angle -64.28^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \text{④ } V_{AN} &= I_{aA} \times Z_{AN} = 2776.1 \angle -64.28^\circ \times (2.352 + j1.11) \\ &= 2776.1 \angle -64.28^\circ \times (2.61 \angle 25.84^\circ) \\ &= 7245.6 \angle -38.44^\circ \text{ Volt} \end{aligned}$$

$$|V_L| = |V_{AB}| = \sqrt{3} \times 7245.6 = 12549.7 \text{ volt}$$

$$(d) S_{3\phi} = 3V_{an} \times I_{aA}^*$$

$$V_{an} = \frac{13800}{\sqrt{3}} \angle -30^\circ - \left[(0.003 + j0.3) \times 2776.1 \angle -64.3^\circ \right]$$
$$= 6145.9 - 4337.2j = 7522.3 \angle -35.2^\circ$$

$$P = 3V_{an} I_{aA} \cos(\theta_V - \theta_I)$$
$$= 3 \times 7522.3 \times 2776.1 \cos(-35.2^\circ - -64.28^\circ)$$
$$= 54.75 \text{ MW}$$

$$Q = 3V_{an} I_{aA} \sin(\theta_V - \theta_I) = 30.44 \text{ MVAR}$$

$$S = P + jQ = 54.75 + j30.44$$
$$= 62.6 \angle 29.07^\circ \text{ MVA}$$


(or)

$$S_{3\phi} = 3 \times 7522.3 \angle -35.2^\circ \times 2776.1 \angle 64.28^\circ$$
$$= 62.6 \angle 29.07^\circ \text{ MVA}$$

$$M = k \sqrt{L_1 L_2}$$

$$M = 0.6 \sqrt{\frac{20}{2000} \times \frac{40}{2000}} = 8.5 \times 10^{-3} \text{ H}$$

$$j\omega M = 17j$$

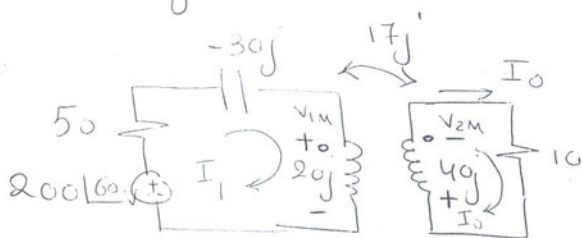

$$200 \angle 60^\circ - (50 - 30j + 20j) \bar{I}_1 - V_{1M} = 0$$

$$V_{1M} = + - \bar{I}_0 (17j)$$

$$(40j + 10) \bar{I}_0 + V_{2M} = 0$$

$$V_{2M} = - + \bar{I}_1 (17j)$$

$$200 \angle 60^\circ - (50 - 10j) \bar{I}_1 + 17j \bar{I}_0 = 0$$

$$(40j + 10) \bar{I}_0 - 17j \bar{I}_1 = 0$$

$$\bar{I}_1 = \frac{(10 + 40j) \bar{I}_0}{17j} =$$

$$200 \angle 0^\circ - \frac{(50 - 10j)(10 + 40j)}{1 + j} I_0 + 17j I_0 = 0$$

$$200 \angle 0^\circ + (-111.46 + 70j) I_0 = 0$$

$$I_0 = \frac{200 \angle 0^\circ}{111.46 - 70j} = \frac{200 \angle 0^\circ}{131.87 \angle -32^\circ}$$

$$= (1.52 \angle 32^\circ) \text{ A}$$

$$I_1 = \frac{10 + 40j}{17j} I_0 = \frac{(10 + 40j)(1.52 \angle 32^\circ)}{17j}$$

$$= (2.39 - 0.52j)(1.52 \angle 32^\circ)$$

$$= 2.422 \angle -14^\circ \times ()$$

$$= (3.68 \angle 78^\circ) \text{ A}$$

$$8 \quad I_0 = 1.52 \cos(2000 \times 10^{-3} \times \frac{180}{\pi} + 32^\circ)$$

$$= -1.36 \text{ A}$$


$$I_1 = 3.68 \cos(2000 \times 10^{-3} \times \frac{180}{\pi} + 78^\circ)$$

$$= -3.6 \text{ A}$$

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_0^2 - M I_1 I_0 = (0.49 \text{ J})$$

$$= \frac{1}{2} \left(\frac{20}{1000} \right) (-3.6)^2 + \frac{1}{2} \left(\frac{40}{1000} \right) (-1.36)^2 - \frac{8.5}{1000} \times (-3.6)(-1.36)$$

at $t < 0$ switch was opened.

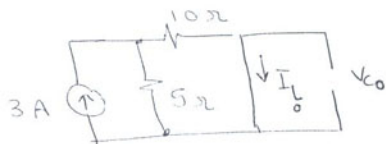

$$I_{L_0} = \frac{3 \times 5}{15} = 1A \quad \text{and} \quad V_{C_0} = 0$$

at $t \geq 0$ switch was closed.

$$\frac{V_0 - \frac{15}{5}}{5} + \frac{V_0 + LI_0}{5L} + V_0 5C = 0$$

$$V_0 \left(\frac{1}{5} + \frac{1}{5L} + 5C \right) = \frac{3}{5} - \frac{I_0}{5} = \frac{3}{5} - \frac{1}{5} = \frac{2}{5}$$

$$\therefore V_0 = \frac{2}{5 \left(\frac{1}{5} + \frac{1}{5L} + 5C \right)} = \frac{10}{\frac{5 \times 5^2}{100} + 5 + 5}$$

$$V_0 = \frac{200}{s^2 + 20s + 100} = \frac{200}{(s+10)^2}$$

~~$$s_{1,2} = -20 \pm \sqrt{400}$$~~

$$V_0(t) = 200t e^{-10t}$$

$$(4) \quad f(t) = f(-t) \rightarrow \text{even} \rightarrow b_n = .$$

$$\frac{T}{2} = 2 \rightarrow T = 4$$

$$f(t) = 1-t \quad 0 < t < 2$$

$$(0,1) \text{ and } (2,-1) \quad \frac{y_2 - y_1}{x_2 - x_1} = \frac{y_2 - y_1}{x_2 - x_1}$$

$$\frac{y-1}{x-0} = \frac{-1-1}{2-0} = \frac{-2}{2} = -1$$

$$y-1 = -x \rightarrow y = 1-x \quad f(t) = 1-t$$

$$a_0 = \frac{2}{T} \int_0^{T/2} f(t) dt = \frac{2}{T} \int_0^{T/2} (1-t) dt$$

$$= \frac{2}{T} \left(t - \frac{t^2}{2} \right) \Big|_0^{T/2} = \frac{2}{T} \left[\left(\frac{T}{2} - 0 \right) - \left(\frac{T^2}{8} - 0 \right) \right]$$

$$= \frac{2}{T} \left(\frac{T}{2} - \frac{T^2}{8} \right) = 1 - \frac{T}{4} = 1 - \frac{4}{4} = 0$$

$$a_n = \frac{2}{T} \int_0^{T/2} f(t) \cos n\omega_0 t dt$$

$$= \frac{4}{T} \int_0^{T/2} (1-t) \cos n\omega_0 t dt$$

$$= \frac{4}{T} \left[\frac{\sin n\omega_0 t}{n\omega_0} - \left(\frac{1}{(n\omega_0)^2} \cos n\omega_0 t + \frac{t}{n\omega_0} \sin n\omega_0 t \right) \right]_0^{T/2}$$


$$= \frac{4}{T} \left[\frac{T}{n2\pi} \left(\sin n\frac{\pi 2}{T} \frac{T}{2} - 0 \right) - \frac{T^2}{(n2\pi)^2} \left(\cos n\frac{2\pi T}{T} - 1 \right) + \frac{T^2}{2n2\pi} \left(\sin n\frac{2\pi T}{T} - 0 \right) \right]$$

$$\omega_0 = \frac{2\pi}{T}$$

$$a_n = 0 - \frac{I}{(n\pi)^2} [(-1)^n \cos(n\pi) - 1] + 0$$

$$V(t) = \underbrace{\left(1 - \frac{I}{4}\right)}_{V_0} + \sum_{n=1}^{\infty} \frac{I}{(n\pi)^2} (1 - \cos n\pi) \cos n\omega t$$
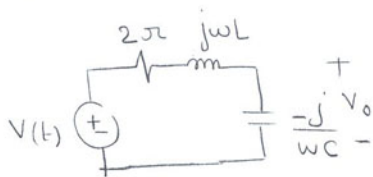
$$V_0(t) = \frac{V(t) \left(\frac{-j}{\omega C}\right)}{2 + j\omega L - \frac{j}{\omega C}}$$



For DC comp: -

$$V_0 = V(t) = 1 - \frac{I}{4} = 1 - \frac{4}{4} = 0$$

For AC comp: -


First non zero terms at $n = 1, 3, 5$

at $n=1$

$$V_0(t) = \frac{\frac{4 \times (2)}{\pi^2} (-j 1.27)}{2 + j \frac{2\pi \times 1}{4} - \frac{j}{2\pi \times 0.5}} = \frac{-1.03j}{2 + 1.57j - j 1.27}$$

$$= \frac{-1.03 \angle 90^\circ}{2 + 0.29j} = \frac{-1.03 \angle 90^\circ}{2.02 \angle 8.25^\circ} = -0.51 \angle 81.75^\circ$$

(5)

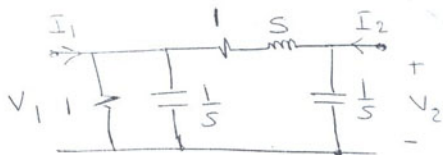


$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \& \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \quad \& \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

 $Z_{11} =$
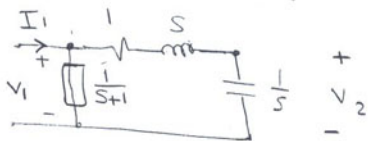
$$Z_{11} = \frac{1 \times \frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s+1}$$



$$\begin{aligned} Z_{11} &= \frac{(s + \frac{1}{s} + 1) \left(\frac{1}{s+1} \right)}{\left(s + \frac{1}{s} + 1 + \frac{1}{s+1} \right)} = \frac{s + \frac{1}{s} + 1}{\left(s + \frac{1}{s} + 1 \right) (s+1) + 1} \\ &= \frac{s^2 + s + 1}{s^3 + 2s^2 + 3s + 1} \end{aligned}$$

$$V_2 = \frac{V_1 \times \frac{1}{s}}{\left(s + \frac{1}{s} + 1 \right)} = \frac{V_1}{s^2 + s + 1}$$


$$I_1 = \frac{V_1}{Z_{11}} = \frac{V_1 (s^3 + 2s^2 + 3s + 1)}{(s^2 + s + 1)}$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{V_1 (s^2 + s + 1)}{(s^2 + s + 1) \frac{V_1 (s^3 + 2s^2 + 3s + 1)}{(s^2 + s + 1)}}$$


$$Z_{21} = \frac{1}{s^3 + 2s^2 + 3s + 1}$$

For $Z_{22} = \frac{V_2}{I_2}$
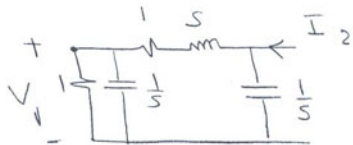
$$Z_{22} = \left[\frac{\left(\frac{1}{s+1} + s+1\right) \times \frac{1}{s}}{\left(\frac{1}{s+1}\right) + 1 + s + \frac{1}{s}} \right]$$


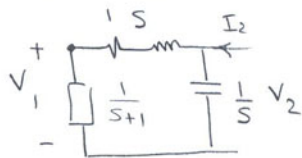
$$= \frac{s(s+1)}{s(s+1)} \left[\right]$$



$$= \frac{1 + (s+1)^2}{s + s(1+s)^2 + s+1}$$

$$= \frac{s^2 + 2s + 2}{s^3 + 2s^2 + 3s + 1}$$

$$V_1 = \frac{V_2 \times \left(\frac{1}{s+1}\right)}{s+1 + \left(\frac{1}{s+1}\right)} = \frac{V_2}{(s+1)^2 + 1} = \frac{V_2}{s^2 + 2s + 2}$$

$$I_2 = \frac{V_2}{Z_{22}} = \frac{V_2 (s^3 + 2s^2 + 3s + 1)}{(s^2 + 2s + 2)}$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{V_2 (s^2 + 2s + 2)}{(s^2 + 2s + 2) V_2 (s^3 + 2s^2 + 3s + 1)}$$

$$= \frac{1}{s^3 + 2s^2 + 3s + 1}$$

$$Z = \begin{bmatrix} \frac{s^2 + s + 1}{s^3 + 2s^2 + 3s + 1} & \frac{1}{s^3 + 2s^2 + 3s + 1} \\ \frac{1}{s^3 + 2s^2 + 3s + 1} & \frac{s^2 + 2s + 2}{s^3 + 2s^2 + 3s + 1} \end{bmatrix}$$