


Time Allowed: 3 Hours

QUESTION 1:

- Show how matrix partitioning can be used in node elimination in power systems. What conditions should be first satisfied?
- Show how tap changing transformers can be used to change the Y-bus of a given Power System.


QUESTION 2:

- Show that $Y_{bus} = A^T Y_{pr} A$
- Calculate the bus admittance matrix for the Power System represented in Fig.1

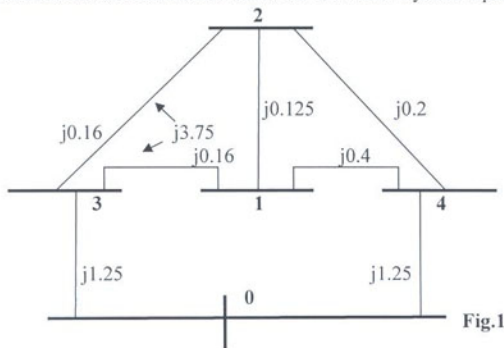

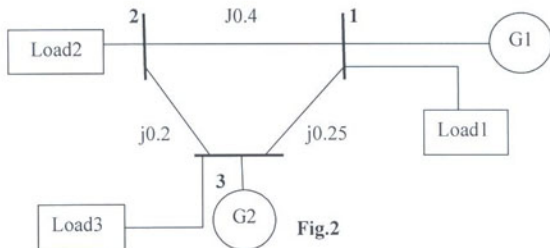QUESTION 3: For the power system shown in Fig.2

- Form the Ybus Matrix
- Perform 2 iterations of the Gauss-Seidel load flow to calculate all missing data at each bus.



Given that:

$V_1=1.02+j0$	$PL_1=0.8$	$QL_1=0.6$	(Slack Bus)	
$PL_2=2.4$	$QL_2=1.8$		(Load Bus)	
$ V_3 =1$	$PG_3=1.5$	$PL_3=0.8$	$QL_3=1.2$	(Voltage Controlled Bus)

$-5 \leq Q_3 \leq 5$.

QUESTION 4: Consider the Power System shown in Fig.3

For a 3phase fault at the middle point of Line1-3, calculate the following:

- Current through the fault
- Voltage at each bus after the fault
- Fault current in each Transmission line.
- Fault Current drawn from each generator.

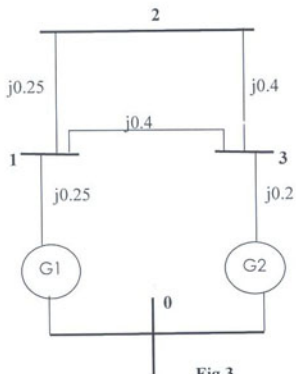


Fig.3

GOOD LUCK

Dr. Wael Ismael

Question 1 [15 Marks] (1)

a) The 2 conditions are:

① We are not interested in the voltage at this bus.

② The current is zero at this bus.

$$\begin{array}{l} \text{Non} \\ \text{zero} \end{array} \left\{ \begin{array}{l} IA \\ \dots \\ IB \end{array} \right\} = \begin{bmatrix} K & L \\ \dots & \dots \\ L^T & M \end{bmatrix} \begin{bmatrix} VA \\ \dots \\ VB \end{bmatrix}$$

$$IA = KVA + LVB$$

$$IB = L^T VA + MVB \quad ; \text{ but } IB = 0$$


$$\therefore VB = -M^{-1} L^T VA$$

$$\therefore IA = KVA - L M^{-1} L^T VA$$


$$IA = \underbrace{[K - L M^{-1} L^T]}_{\text{New } Y_{bus}} VA$$

(5) Marks

(b)

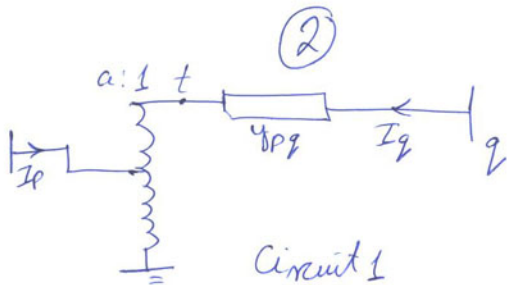

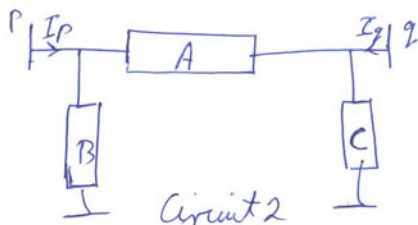It is required to represent the "Transformer T.L" system by an equivalent π section as follows.



$$\frac{E_p}{E_t} = \frac{a}{1} \quad \therefore \frac{I_p}{I_t} = \frac{1}{a} \quad \therefore I_t = a I_p$$

from circuit ① $I_t = [E_t - E_q] Y_{pq}$

$$a I_p = [E_p - E_q] Y_{pq}$$

$$\therefore I_p = E_p \frac{Y_{pq}}{a^2} - \frac{Y_{pq}}{a} E_q \quad \text{I}$$

$$\begin{aligned} I_q &= (E_q - E_t) Y_{pq} \\ &= (E_q - \frac{E_p}{a}) Y_{pq} \end{aligned}$$

$$\therefore I_q = -\frac{Y_{pq}}{a} E_p + Y_{pq} E_q \quad \text{II}$$

(3)

from circuit 2

$$I_p = (E_p - E_q)A + E_p B$$

$$\therefore I_p = (A+B)E_p + A E_q \quad \text{III}$$

$$I_q = -A E_p + (A+C) E_q \quad \text{IV}$$

Equating I & III ; II & IV


$$\therefore A = \frac{y_{p2}}{a} ; B = \frac{y_{p2}}{a} \left(\frac{1}{a} - 1 \right)$$

$$C = y_{q2} \left(1 - \frac{1}{a} \right)$$

$$Y_{pp} = y_{p1} + y_{p2} + \dots + (A+B)$$

$$Y_{pq} = Y_{qp} = -A$$
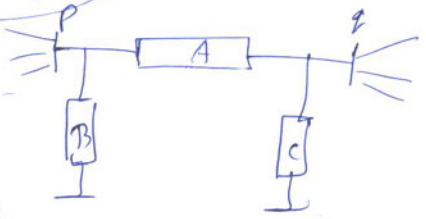
$$Y_{qq} = y_{q1} + y_{q2} + \dots + (A+C)$$




$$\therefore [Y_{bus \text{ modified}}] = \begin{bmatrix} Y_{11} & Y_{12} & \dots & Y_{1n} \\ Y_{21} & Y_{22} & \dots & Y_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{p1} & Y_{p2} & \dots & Y_{pn} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{q1} & Y_{q2} & \dots & Y_{qn} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{n1} & Y_{n2} & \dots & Y_{nn} \end{bmatrix}$$

(10) Marks

Question 2 **15 Marks** (4)

(a) Assume the following system:

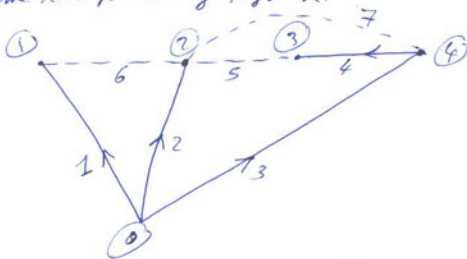

$$A = \begin{bmatrix} -1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 \\ 0 & 1 & -1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \end{bmatrix}$$

$$\begin{aligned} \mathcal{V}_1 &= -V_1; \mathcal{V}_2 = -V_2; \mathcal{V}_3 = -V_4 \\ \mathcal{V}_4 &= V_4 - V_3; \mathcal{V}_5 = V_2 - V_3 \\ \mathcal{V}_6 &= V_1 - V_2; \mathcal{V}_7 = V_2 - V_4 \end{aligned}$$

$$\therefore [I_{pr}] = A[V]$$

$$I_1 = -I_1 + I_6; I_2 = -I_2 + I_5 - I_6 + I_7$$

$$I_3 = -I_4 - I_5 \quad I_4 = -I_3 + I_4 - I_7$$

$$\therefore A^T I_{pr} = I$$

$$\mathcal{V}_{pr} = Y_{pr} I_{pr}$$

$$\therefore (Y_{pr})^{-1} \mathcal{V}_{pr} = I_{pr} \quad \therefore I_{pr} = Y_{pr} \mathcal{V}_{pr}$$

$$\therefore A^T Y_{pr} \mathcal{V}_{pr} = A^T I_{pr}$$

$$\therefore A^T Y_{pr} \mathcal{V}_{pr} = I$$

$$\therefore \underbrace{A^T Y_{pr} A}_{V} = I$$

(7) Marks

(5)

(b)

$$A = \begin{bmatrix} 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & -1 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & 1 \\ 1 & 0 & 0 & -1 \\ 1 & -1 & 0 & 0 \end{bmatrix}$$

$$Z_{pr} = \begin{bmatrix} j1.25 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & j1.25 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & j0.16 & j3.75 & 0 & 0 & 0 \\ 0 & 0 & j3.75 & j0.16 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & j0.2 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & j0.4 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & j0.125 \end{bmatrix}$$

$$\therefore Y_{pr} = Z_{pr}^{-1} = \begin{bmatrix} -j0.8 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -j0.8 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & +j0.014 & -j0.267 & 0 & 0 & 0 \\ 0 & 0 & -j0.267 & +j0.014 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 15 & j0.5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -j8 \end{bmatrix}$$

6

$$Y_{bus} = A^T Y_{\text{per}} A$$

$$= \begin{bmatrix} -j10.4886 & j7.7328 & j0.2558 & j2.5 \\ j7.7328 & -j12.9886 & j0.2558 & j5 \\ j0.2558 & j0.2558 & -j1.3116 & 0 \\ j2.5 & j5 & 0 & -j8.3 \end{bmatrix}$$

(8) Marks

(7)

Question 3 20 Marks

$$(a) Y_{bus} = \begin{bmatrix} -j6.5 & j2.5 & j4 \\ j2.5 & -j7.5 & j5 \\ j4 & j5 & -j9 \end{bmatrix}$$

(5) Marks

$$(b) V_2^{(1)} = \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{V_2^{(0)*}} - Y_{21} V_1^{(0)} - Y_{23} V_3^{(0)} \right]$$

$$= \frac{-1}{j7.5} \left[\frac{-24 + j1.8}{1} - j2.5 \times 1.02 - j5 \times 1 \right]$$

$$= 0.7667 - j0.32$$

$$Q_3^{(1)} = -\text{Im} \left[E_3^{(0)*} \left[Y_{31} E_1 + Y_{32} E_2^{(1)} + Y_{33} E_3^{(0)} \right] \right]$$

$$= -\text{Im} \left[1 \left(j4 \times 1.02 + j5 (0.7667 - j0.32) - j9 \times 1 \right) \right]$$

$$= -\text{Im} [1.6 - j1.0865]$$

$$\therefore Q_3^{(1)} = 1.0865$$

$$\therefore Q_{3g} = Q_3^{(1)} + Q_{L3} = 2.2865$$

$$\therefore -5 < 2.2865 < 5$$

\(\therefore\) in range

$$\begin{aligned} \therefore V_3^{(1)} &= \frac{1}{Y_{33}} \left[\frac{P_3 - jQ_3}{V_3^{(1)*}} - Y_{31} V_1^{(0)} - Y_{32} V_2^{(1)} \right] \\ &= 1 - j0.1 \\ \therefore \delta_3^{(1)} &= -5.71 \end{aligned}$$

$$\therefore V_3^{\text{corrected}} = 1 \angle -5.71$$

$$\begin{aligned} V_2^{(2)} &= \frac{1}{Y_{22}} \left[\frac{P_2 - jQ_2}{V_2^{(2)*}} - Y_{21} V_1 - Y_{23} V_3^{(1)} \right] \\ &= 0.6653 \angle -27.82 \end{aligned}$$

$$\begin{aligned} Q_3^{(2)} &= -\text{Im} \left[V_3^{(1)*} \left[Y_{31} V_1^{(0)} + Y_{32} V_2^{(2)} + Y_{33} V_3^{(1)} \right] \right] \\ &= 1.8549 \end{aligned}$$

$$\begin{aligned} \therefore Q_{3g} &= 1.8549 + Q_{L3} = 3.0549 \\ -5 &\leq 3.0549 \leq 5 \end{aligned}$$

$$\therefore V_3^{(2)} = 0.8998 - j0.1091$$

$$\therefore \delta_3^{(2)} = -7.23$$

$$\therefore V_3^{\text{corrected}} = 1 \angle -7.23 = 0.99205 - j0.126$$


$$\begin{aligned} P_1 - jQ_1 &= V_1^* \left[Y_{11} V_1^{(0)} + Y_{12} V_2^{(2)} + Y_{13} V_3^{(2)} \right] \\ &= 1.3308 - j1.2174 \end{aligned}$$

$$P_1 = P_{G1} - P_{L1} \quad \therefore P_{G1} = 2.1308 \text{ pu}$$

$$Q_{G1} = 1.817 \text{ pu} \quad (15) \text{ Marks}$$

(9)

Question 4: 20 Marks

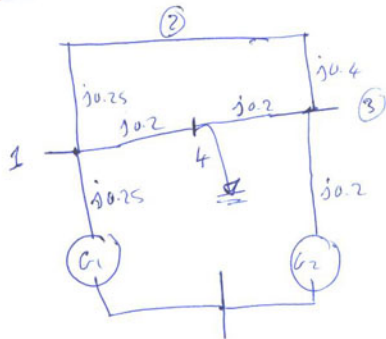

$$Y_{bus} = \begin{bmatrix} -j13 & j4 & 0 & j5 \\ j4 & -j6.5 & j2.5 & 0 \\ 0 & j2.5 & -j12.5 & j0.5 \\ j5 & 0 & j5 & -j10 \end{bmatrix}$$

$$Z_{bus} = [Y_{bus}]^{-1} = \begin{bmatrix} j0.1604 & j0.1263 & j0.0717 & j0.116 \\ j0.1263 & j0.2696 & j0.0991 & j0.1127 \\ j0.0717 & j0.0991 & j0.1426 & j0.1072 \\ j0.116 & j0.1127 & j0.1072 & j0.2116 \end{bmatrix}$$

Fault Bus

(10) Marks

(10)

Note: Z_{bus} may be also determined by direct Method

$$I_f = \frac{V_f}{Z_{44}} = \frac{1}{j0.2116} = -j4.726 \text{ p.u.}$$

$$V_{1f} = V_f \left(1 - \frac{Z_{14}}{Z_{44}}\right) = 0.4518 \text{ p.u.}$$

$$V_{2f} = V_f \left(1 - \frac{Z_{24}}{Z_{44}}\right) = j0.4674 \text{ p.u.}$$

$$V_{3f} = V_f \left(1 - \frac{Z_{34}}{Z_{44}}\right) = 0.4934 \text{ p.u.}$$

$$I_{f(1-2)} = \frac{V_{1f} - V_{2f}}{Z_{12}} = -j0.0624 \text{ p.u.}$$

$$I_{f(1-4)} = \frac{V_{1f} - 0}{j0.2} = -j2.259 \text{ p.u.}$$

$$I_{f(2-3)} = \frac{V_{2f} - V_{3f}}{j0.4} = -j0.065 \text{ p.u.}$$

$$I_{f(3-4)} = \frac{0.4934 - 0}{j0.2} = -j2.467 \text{ p.u.}$$

$$I_{fG1} = \frac{1 - 0.4518}{j0.25} = -j2.1928 \text{ p.u.}$$

$$I_{fG2} = \frac{1 - 0.4674}{j0.2} = -j2.533 \text{ p.u.}$$

(10) Marks