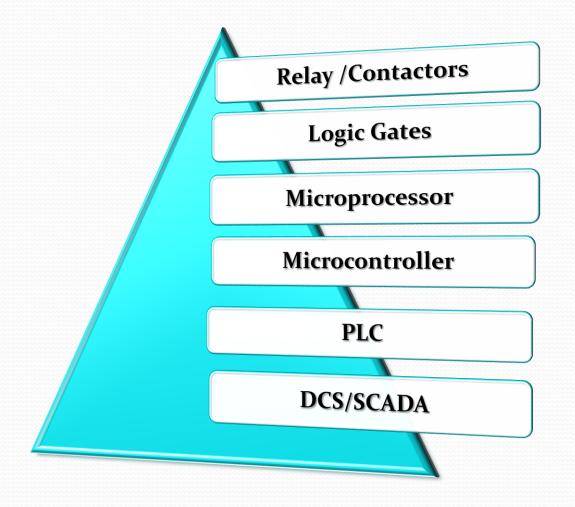


Control History



Eng / Ahmad Gamal Ahmad

Principles of Automatic Control





What are the types of switches ??

Switches


Manually Operated Switches

Mechanically
Operated
Switches

Manually Operated Switches

Toggle Switches

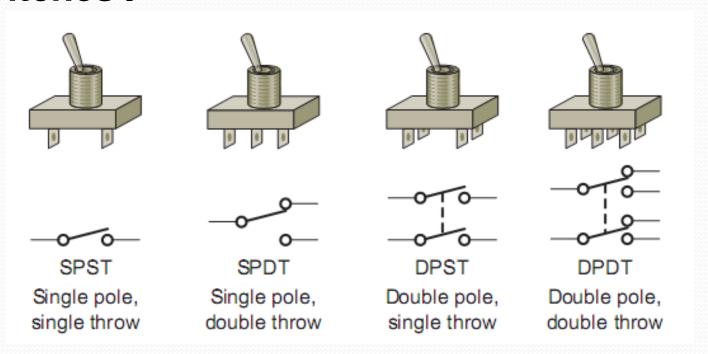
Toggle Switches are manually operated switches.




Eng / Ahmad Gamal Ahmad

- Pushbutton Switches(PB)
- Pushbuttons are manually operated switches.
- A push button operates by pressing a button that opens or closes contacts.
- ✓ Abbreviations N.O. (normally open) and N.C. (normally closed) represent the state of the switch contacts when the switch is not activated.

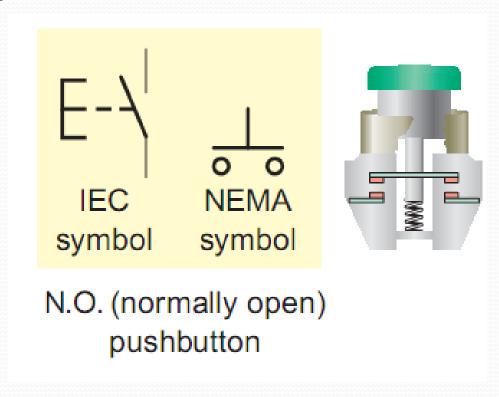✓ The NO PB makes a circuit when it is pressed and returns to its open position when the button is released.



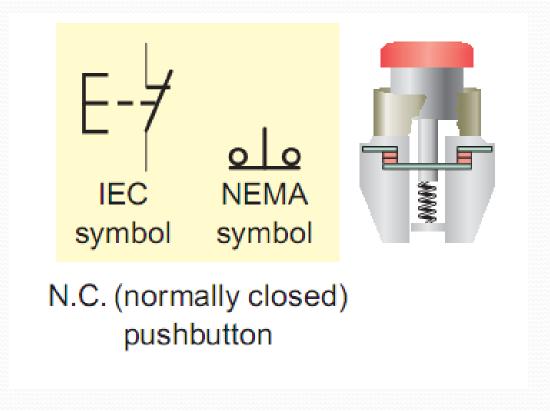The N.C. PB opens the circuit when it is pressed and returns to the closed position when the button is released.



Eng / Ahmad Gamal Ahmad



Pushbutton station—NEMA Type1.

NEMA: National Electrical Manufacturers Association

Eng / Ahmad Gamal Ahmad

- Selector Switches
- Selector Switches are manually operated switches.

- These switches may have two or more selector positions.
- Switch positions are established by turning the operator knob right or left.





Selector switch

Eng / Ahmad Gamal Ahmad

Mechanically Operated Switches

Limit Switches

- Limit switches are mechanically operated switches
- Limit switch is controlled automatically by factors such as pressure, position, and temperature.

N.O.




Eng / Ahmad Gamal Ahmad

Pressure Switches

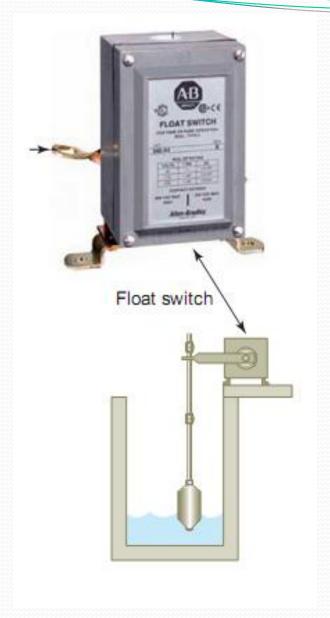- Pressure Switches are mechanically operated switches
- Pressure Switches are used to monitor and control the pressure of liquids and gases.





Eng / Ahmad Gamal Ahmad




Eng / Ahmad Gamal Ahmad

Electromechanical Control Relays

- ➤ Electromechanical Relay (EMR) is a switch operated by an electromagnet.
- > EMR consists of two circuits:
- 1) The Input /Coil /Control Circuit
- 2) The Output / Load /Power Circuit



Relay Operation

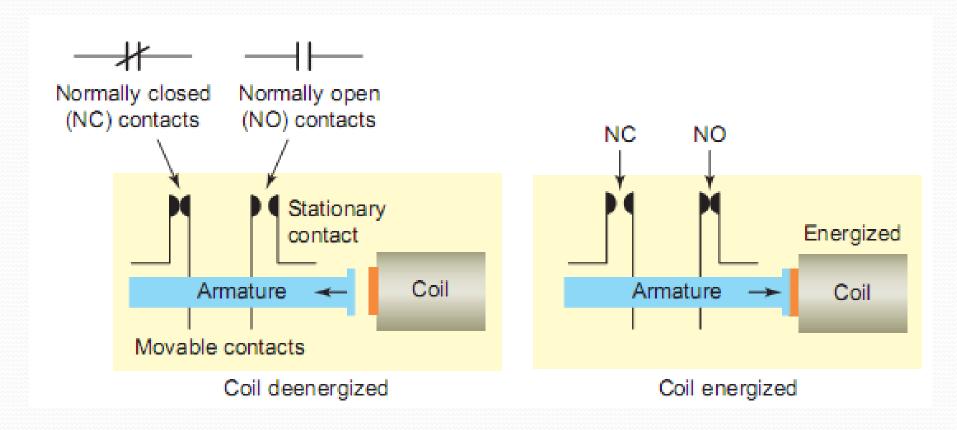

Eng / Ahmad Gamal Ahmad

Relay Operation

- When the coil is energized, it produces an electromagnetic field.
- Action of this field, in turn, causes the armature to move, closing the NO contacts and opening the NC contacts.

The distance that the plunger moves is generally short—about ¼ inch or less.


- Normally open contacts are open when no current flows through the coil but closed as soon as the coil conducts a current or is energized.
- Normally closed contacts are closed when the coil is deenergized and open when the coil is energized.

Relay Applications

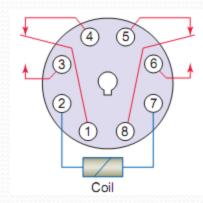Relays are used to control small loads of small electrical signal(0-15 A & 220/480V)








- It desired to control the temperature the of the an oven as follows:
- Position A
- when the temperature exceeds the setting value the cooling fans start running
- 2) when the temperature drops below the setting value the cooling fans stop running
- Position M the cooling fans run manually without the temperature sensor with start and stop PB.

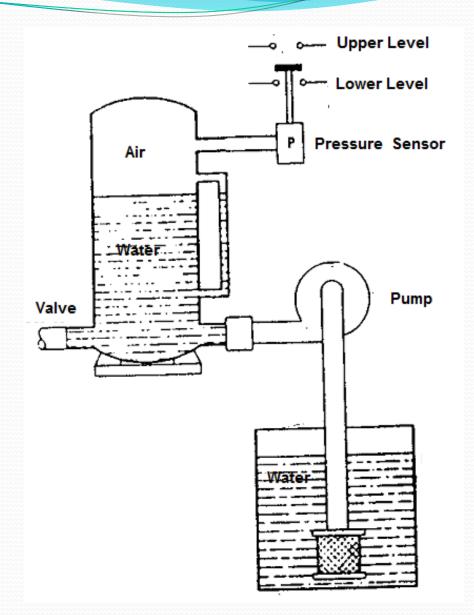- when the pressure reaches The lower level the pump runs and continues running till the pressure reaches the upper limit.
- when the pressure reaches the Upper limit the pump stops running and so on.



- It is desired to control the operation of the pump in the previous application using a selector of 2 positions
- Position M: the pump operates manually without the pressure sensor with start and stop PB.
- 2) Position A: the pump operates automatically with the pressure sensor.

- when the water level reaches B2the pump runs and continues running till the water level reaches B1
- when the water level reaches B1 the pump stops running and does not run till the water level reaches B2 and so on .
- ➤B1 & B2 have normally open contacts

